



**National 5  
Physics**

**Solutions to  
Electricity & Energy  
exam questions**

1. (a)

$$I = \frac{P}{V} \quad (1)$$

$$= \frac{60}{230} \quad (1)$$

$$= 0.26 \text{ A} \quad (1) \quad [\text{number **and** unit must be correct}]$$

3

(b) (i)

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} \quad (1)$$

$$\frac{1}{R_T} = \frac{1}{46} + \frac{1}{92} \quad (1)$$

$$R_T = 30.67 \, \Omega \quad (1) \quad [\text{number **and** unit must be correct}]$$

3

(ii)

$$P = \frac{V^2}{R} \quad (1)$$

$$= \frac{230^2}{30.67} \quad (1)$$

$$= 1725 \text{ W} \quad (1) \quad [\text{number **and** unit must be correct}]$$

3

[or calculate individual power of each heating element and add together]

(iii) S3 (only) 1

(iii) Greatest value of resistance 1

OR

lowest current

OR

lowest power

2. (a)

$$I = \frac{V}{R} \quad (1)$$

$$= \frac{12}{64000}$$

$$= 1.875 \times 10^{-4} \text{ (A)} \quad (1) \text{ for correct current}$$

THEN

$$V = IR \quad [\text{no mark for reuse of Ohm's Law}]$$

$$= 1.875 \times 10^{-4} \times 4000$$

$$= 0.75 \text{ V}$$

(1) [number **and** unit must be correct]

3

(b) Transistor (switch)

(1)

1

(c)

- R of LDR increases (1)
- V across LDR increases (1)
- (above 0.7V) Transistor switches ON (1)
- Relay coil is energised (1)  
(which closes the relay switch and activates the motor)

4

3. (a)  $c = 4180 \text{ (J Kg}^{-1} \text{ C}^{-1}\text{)}$  (1) full marks only possible when correct value from datasheet is used.
- $E_h = c m \Delta T$  (1)
- $= 4180 \times 1.6 \times 80$  (1) 4
- $= 535040 \text{ J}$  (1) [number **and** unit must be correct]
- (b) (i)  $E_h = mL$  (1)
- $E_h = 0.9 \times 22.6 \times 10^5$  (1) for correct L value from datasheet
- (1) both substitutions correct
- $E_h = 2.034 \times 10^6 \text{ J.}$  (1) [number **and** unit must be correct] 4
- (ii)  $P = \frac{E}{t}$  (1)
- $2000 = \frac{2.034 \times 10^6}{t}$  (1)
- $t = 1017 \text{ s}$  (1) [number **and** unit must be correct] 3

4.

$$E_p = m g h \quad (1)$$

$$= 25 \times 9.8 \times 1.2 \quad (1)$$

$$= 290 \text{ J} \quad (1)$$

[number **and** unit must be correct]

3

5	(a)	(i)	$(33-21) = 12 \text{ }^\circ\text{C}$	(1)	[number <b>and</b> unit must be correct]	1
		(ii)	$(120,000-12,000) = 108,000 \text{ J}$	(1)	[number <b>and</b> unit must be correct]	1
		(iii)	$E_h = cm\Delta T$ $108,000 = c \times 2.0 \times 12$ $c = 4,500 \text{ J kg}^{-1} \text{ }^\circ\text{C}^{-1}$	(1) (1) (1)	[number <b>and</b> unit must be correct]	3
(b)	(i)	Any <b>two</b> of the following;				
		Measured value of $E_h$ too large	(1)			
		OR				
		$\Delta T$ too small	(1)			
		OR				
Heat lost to surroundings (or similar)	(1)					
OR						
water not evenly heated (or similar)	(1)		2			
(b)	(ii)	Insulate beaker				
		<b>OR</b>				
		Put lid on beaker				
		<b>OR</b>				
		Stir water				
<b>OR</b>						
Fully immerse heater			1			
(c)		$E = P t$	(1)			
		$108,000 = P \times (5 \times 60)$	(1)			
		$P = 360 \text{ W}$	(1)	[number <b>and</b> unit must be correct]	3	

6 (a)  $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$  (1)

$$= \frac{1}{4} + \frac{1}{2}$$
 (1)

$$\therefore R_T = 1.3 \Omega$$
 (1) [number **and** unit must be correct]

3

(b)  $R_T = R_1 + R_2$  (1)

$$= 1.3 + 6$$
 (1)

$$= 7.3 \Omega$$
 (1) [number **and** unit must be correct]

3

(c) (Voltage across 2  $\Omega$  resistor = Voltage across 4  $\Omega$  resistor)

$$V = IR$$
 (1)

$$= 0.1 \times 4 \text{ (or } 0.2 \times 2)$$
 (1)

$$= 0.4 \text{ V}$$
 (1) [number **and** unit must be correct]

3

- 7 (a) dc – electrons flow (or current flows) around a circuit in one direction only (1)
- ac – electrons' (or current) direction changes/reverses after a set time (1)

2



8. (a) To reduce current in LED 1  
**OR**  
To reduce voltage across LED

(b)  $V = 6 - 2 = 4 \text{ V}$  (1)

$V = IR$  (1)

$4 = 0.1 \times R$  (1)

$R = 40 \ \Omega$  (1) [number **and** unit must be correct] 4

(c)  $P = I^2R$  OR  $P = V^2/R$  (1)

$= (0.1)^2 \times 40$   $= \frac{4^2}{40}$  (1)

$= 0.4 \text{ W}$   $= 0.4 \text{ W}$  (1) [number **and** unit must be correct] 3

OR

$P = IV$  (1)

$= 0.1 \times 4$  (1)

$= 0.4 \text{ W}$  (1) [number **and** unit must be correct]

**9.** D

**10.** E

**11.** B

**12.** A

**13.** E

**14.** A

15. (a) (i)  $P = I V$  (1)  
 $36 = I \times 12$  (1)  
 $I = 3 \text{ A}$  (1) [number **and** unit must be correct] 3
- (ii)  $48 = 12 + 12 + V_R$   
 $V_R = 24 \text{ V}$  (1) [number **and** unit must be correct] 1
- (iii)  $V = I R$  (1)  
 $24 = 3 \times R$  (1)  
 $R = 8 \Omega$  (1) [number **and** unit must be correct] 3
- (b) (i)  $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$  (1)
- $\frac{1}{R_T} = \frac{1}{6} + \frac{1}{4} + \frac{1}{4}$  (1)
- $\frac{1}{R_T} = 0.17 + 0.25 + 0.25$
- $R_T = 1.5 \Omega$  (1) [number **and** unit must be correct] 3
- (ii) A. The reading decreases/gets smaller/reduces (1) 1
- B. The resistance increases (so the current decreases) (1) 1

16. (a) Use Ohm's Law twice.  
Once to calculate the current, then once to find  $V_R$ .

$$V = I R \quad (1)$$

$$0.36 = I \times 2000$$

$$I = 0.00018 \text{ (A)}$$

$$V = I R \quad [\text{no mark for using equation again}]$$

$$= 0.00018 \times 4800 \quad (1) \text{ for both substitutions}$$

$$= 8.64 \text{ V} \quad (1) \quad [\text{number and unit must be correct}]$$

3

- (b)

$$P = \frac{V^2}{R} \quad (1)$$


$$3 = \frac{V^2}{48} \quad (1)$$

$$V^2 = 144$$

$$V = 12 \text{ V} \quad (1) \quad [\text{number and unit must be correct}]$$

3

17. (a)

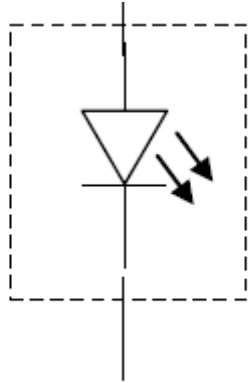

1

- (b) Protect the LED OR prevent damage to the LED  
OR  
limits the current  
OR  
reduces voltage across LED

1

(c)

$$V_R = 6 - 1.2 = 4.8 \text{ V} \quad (1)$$

$$V = IR \quad (1)$$

$$4.8 = 15 \times 10^{-3} \times R \quad (1)$$

$$R = 320 \text{ } \Omega \quad (1)$$

[number **and** unit must be correct]

4

18.

$$P = I^2 R \quad (1)$$

$$= (200 \times 10^{-3})^2 \times 20 \quad (1)$$

$$= 0.8 \text{ W} \quad (1) \text{ [number **and** unit must be correct]}$$

3

19. (a)  $E = Pt$  (1)  
 $= 1500 \times 35$  (1)  
 $= 52\,500 \text{ J}$  (1) [number **and** unit must be correct] 3
- (b)  $E = cm\Delta T$  (1)  
 $52\,500 = 902 \times m \times (200 - 24)$  (1)  
 $m = 0.33 \text{ kg}$  (1) [number **and** unit must be correct] 3
- (c) Heat is 1
- Lost OR
  - Radiated OR
  - escapes OR
- from the sole plate

**20.** C

**21.** D


**22.** D

**23.** E



24. (a) (i)  $E_p = m g h$  (1)
- $E_p = 0.50 \times 9.8 \times 19.3$  (1)
- $E_p = 95 \text{ J}$  (1) 3
- (ii)  $E_c = c m \Delta T$  (1) [number **and** unit must be correct]
- $95 = 386 \times 0.50 \times \Delta T$  (1)
- $\Delta T = 0.5 \text{ }^\circ\text{C}$  (1) [number **and** unit must be correct] 3
- (iii) Less than. (1)
- Some heat is lost to surroundings/ or equivalent. (1) 2
- (b)  $E_h = mL$  (1)
- $E_h = 0.5 \times (2.05 \times 10^5)$  (1)
- $E_h = 1.025 \times 10^5 \text{ J}$  (1) [number **and** unit must be correct] 3

25. (a)

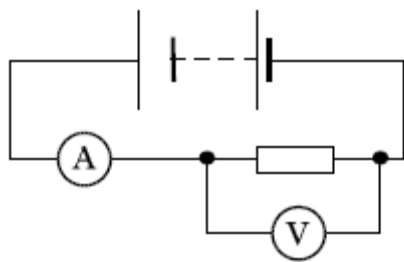

Ammeter in series (1)  
Voltmeter in parallel with resistor (1)  
Battery (not cell) symbol (1)

3

(b)

$$V = IR \quad (1)$$

$$5.7 = 0.60 \times R \quad (1)$$

$$R = 9.5 \Omega \quad (1)$$

[number **and** unit must be correct]

3

(c)

Power rating of resistor = 3 W

1

Power developed in resistor is

$$P = IV \quad (1)$$

$$P = 0.6 \times 5.7 \quad (1)$$

$$P = 3.42 \text{ W} \quad (1)$$

The power rating of the resistor is too low for these current & voltage values. (1)

4

(d)

No, the student is not correct. (1)

In parallel the voltage across each resistor is still the same (1)

OR

6V across each resistor so power is the same (1)

2

- 26 (a) MOSFET (1) 1
- (b) Voltage decreases (1) 1
- (c) (i)  $V_S = V_T + V_{RV}$   
 $12 = 2 \cdot 4 + V_{RV}$   
 $V_{RV} = 9 \cdot 6 \text{ V}$  (1) [number **and** unit must be correct]
- (ii)  $\frac{V_T}{V_{RV}} = \frac{R_T}{R_V}$  (1)
- $\frac{2 \cdot 4}{9 \cdot 6} = \frac{5600}{R_V}$  (1)
- $R_V = 22400 \text{ V}$  (1) [number **and** unit must be correct] 3
- (d) The lamp stays on. (1)
- When temperature decreases,  $R_T$  increases (1)
- Increase in  $R_T$  will increase voltage across the thermistor ( $V_T$ ). (1) 3
- (so MOSFET does not switch off)

27. (a) Parallel (1) 1

(b)  $P = I V$  (1)  
 $300 = I \times 230$  (1)  
 $I = 1.3 \text{ A}$  (1) [number **and** unit must be correct]

OR

$P = I V$  (1)  
 $900 = I \times 230$   
 $I = 3.9 \text{ A}$

Current in one mat =  $3.9 \div 3$  (1)  
 $I = 1.3 \text{ A}$  (1) [number **and** unit must be correct] 3

(c)  $P_{\text{total}} = 3 \times 300 \text{ W} = 900 \text{ W}$

$P = V^2 / R$  (1)  
 $900 = 230^2 / R$  (1)  
 $R = 59 \Omega$  (1) [number **and** unit must be correct]


OR

$I_{\text{total}} = 3 \times 1.3 = 3.9 \text{ A}$

$P = I^2 R$  (1)  
 $900 = 3.9^2 \times R$  (1)  
 $R = 59 \Omega$  (1) [number **and** unit must be correct] 3

28. (a)

1

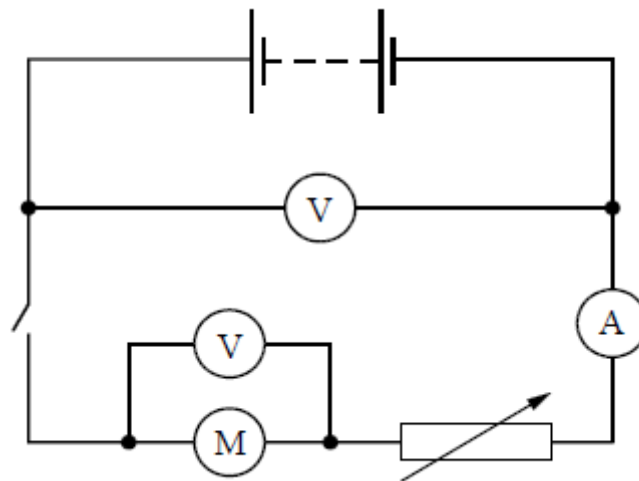

(b)  $V_r = V_s - V_{\text{motor}}$

$$= 24 - 18$$

$$= 6 \text{ (V)} \quad (1)$$

$$V_r = I R \quad (1)$$

$$6 = I \times 2.1 \quad (1)$$

$$I = 2.9 \text{ A} \quad (1) \quad [\text{number and unit must be correct}]$$

4

(c)  $Q = I \times t \quad (1)$

$$= 3.2 \times (10 \times 60 \times 60) \quad (1)$$

$$= 115\,200 \text{ C} \quad (1) \quad [\text{number and unit must be correct}]$$

3

29.  $t = 1/250 = 0.004(\text{s})$  (1)

$E = P t$  (1)

$60 \times 10^{-3} = P \times 0.004$  (1)

$P = 15 \text{ W}$  (1) [number **and** unit must be correct]

4

OR

$E_{\text{Total}} = 250 \times 60 \times 10^{-3} (\text{J})$  (1)

$E = P t$  (1)

$15 = P \times 1$  (1)

$P = 15 \text{ W}$  (1) [number **and** unit must be correct]

30. (a) Transistor 1
- (b)
- (As temp increases,) input voltage to transistor increases (1)
  - (above 0.7V) switching transistor on (1)
  - Current in the (relay) coil produces magnetic field to close switch. (1)
- 3
- (c)  $\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2}$  (1)
- $\frac{1}{R_t} = \frac{1}{16} + \frac{1}{16}$  (1)
- 3
- $R_t = 8 \Omega$  (1) [number **and** unit must be correct]

31. (a)  $E_h = cm\Delta T$  (1)  
 $= 4320 \times 82 \times 125$  (1)  
 $= 44\,280\,000 \text{ J}$  (1) [number **and** unit must be correct] 3

(b)  $E_h = 60\%$  of the heat energy is used  
 $E_h = 44\,280\,000 \times 0.6 = 26\,568\,000 \text{ J}$  (1)

$E_h = mL$  (1)

$26\,568\,000 = m \times (3.42 \times 10^5)$  (1)

$m = 77.7 \text{ kg}$  (1) [number **and** unit must be correct]



32. (a) Lamp A (1)
- It has the lowest resistance/highest current/greatest power (1) 2
- (b)  $P = V^2/R$  (1)
- $= 24^2/2$  (1)
- $= 230 \text{ W}$  (1) [number **and** unit must be correct] 3
- (c)
- 
- 1
- (d) (i) 12 V 1
- (ii)  $1/R_p = 1/R_1 + 1/R_2$  (1)
- $= 1/8 + 1/24$  (1)
- $R_p = 6 \Omega$  (1) [number **and** unit must be correct] 3
- (e) The motor speed will reduce (1)
- The (combined) resistance (of the circuit) is now higher (1)
- OR
- current is lower (1)
- OR
- Voltage across motor is less (1)
- OR
- Motor has less power (1) 2

33. (a) (i) transistor 1
- (ii) To act as a switch 1
- (b) Resistance of LDR reduces, so voltage across LDR reduces (1)  
 Voltage across variable resistor/R increases (1)  
 When voltage across variable resistor/R reaches 0.7 V transistor switches buzzer on. (1) 3
- (c) 80 units: resistance of LDR = 2500 ( $\Omega$ )  
 Total resistance = 2500 + 570  
 = 3070 ( $\Omega$ ) (1)  
 -----  
 $I = V/R$  (1)  
 = 5/3070 (1)  
 =  $1.63 \times 10^{-3}$  A or 1.63 mA (1) [number and unit must be correct] 4
- (d) To set the light level at which the transistor will switch on  
 OR  
 To set the level at which the buzzer will sound 1

**34.** A

**35.** A

**36.** C

**37.** B

**38.** C

**39.** C

40.  $P = \frac{F}{A}$  (1)

$$1 \cdot 01 \times 10^5 = \frac{262}{A} \quad (1)$$

$$A = 2 \cdot 59 \times 10^{-3} \text{ m}^2 \quad (1) \text{ [number and unit must be correct]}$$

3

**41.** B

**42.** C

**43.** A

**44.** B

45. (a) (i)  $P = \frac{F}{A}$  (1)

$$4 \cdot 6 \times 10^5 = \frac{F}{3 \times 10^{-2}} \text{ (1)}$$

$$F = 13\,800 \text{ N} \quad \text{(1) [number and unit must be correct]}$$

(ii)  $P_1 V_1 = P_2 V_2$  (1)

$$(4 \cdot 6 \times 10^5) \times (1 \cdot 6 \times 10^{-3}) = (1 \cdot 0 \times 10^5) \times V_2 \text{ (1)}$$

$$V_2 = 7 \cdot 36 \times 10^{-3} \text{ m}^3 \quad \text{(1) [number and unit must be correct]}$$

46. When the volume of a gas decreases,

- the distance to the walls of the container decreases (1)
- 
- gas particles collide with the walls more often/frequently (1)
- 
- the increased collision rate increases the force on the walls, so pressure is increased. (1)

3

47. When the temperature of a gas is increased,

- the gas particles gain kinetic energy (1)
- 
- and collide with the walls more often/frequently AND  
each collision exerts a greater force on the container walls (1)
- the increased force results in increased gas pressure. (1)

3



**48.** D

48. (a)  $P_1V_1 = P_2V_2$  (1)

$$(750 \times 10^3) \times (8.0 \times 10^{-2}) = (125 \times 10^3) \times V_2 \quad (1)$$

$$V_2 = 0.48 \text{ m}^3 \quad (1) \text{ [number and unit must be correct]}$$

(b) Volume of cylinder =  $8.0 \times 10^{-2} \text{ m}^3$

total volume of gas available to fill balloons  
 $= 0.48 - 0.08 = 0.4 \text{ m}^3$  (1)

number of balloons filled =  $0.4 \div 0.02$  (1)

= 20 balloons (1)