

Unit 3: Electricity

3.2 Circuits

1. 6J of energy is given to each coulomb of charge that passes through the battery.

$$\begin{array}{ll} 2 & V = 1.5V \\ & Q = 12C \\ & W = ? \end{array} \qquad \begin{array}{l} W = QV \\ W = 12 \times 1.5 \\ \underline{W = 18J} \end{array}$$

$$\begin{array}{ll} 3 & V = 12V \\ & Q = 1.6 \times 10^{-19} C \\ & W = ? \end{array} \qquad \begin{array}{l} W = QV \\ W = 1.6 \times 10^{-19} \times 12 \\ \underline{W = 1.92 \times 10^{-18} J} \end{array}$$

$$\begin{array}{ll} 4 & W = 480J \\ & Q = 16C \\ & V = ? \end{array} \qquad \begin{array}{l} W = QV \\ 480 = 16 \times V \\ \underline{V = 30V} \end{array}$$

$$\begin{array}{ll} 5(a) & W = 24J \\ & Q = 0.8C \\ & V = ? \end{array} \qquad \begin{array}{l} W = QV \\ 24 = 0.8V \\ \underline{V = 30V} \end{array}$$

$$\begin{array}{ll} (b) & Q = 12 \times 10^{-6} C \\ & W = 7.2J \\ & V = ? \end{array} \qquad \begin{array}{l} W = QV \\ 7.2 = 12 \times 10^{-6} \times V \\ V = 600,000V \\ \underline{V = 600KV \text{ or } 6 \times 10^5 V} \end{array}$$

6(a) $Q = 48 \times 10^{-3} \text{ C}$

$V = 6 \text{ V}$

$W = ?$

$W = QV$

$W = 48 \times 10^{-3} \times 6$

$W = 0.288 \text{ J}$

$W = 0.29 \text{ J}$

(b) $Q = 500 \times 10^{-6} \text{ C}$

$V = 1.5 \text{ V}$

$W = ?$

$W = QV$

$W = 500 \times 10^{-6} \times 1.5$

$W = 7.5 \times 10^{-4} \text{ J}$

(c) $V = 3 \text{ V}$

$Q = 1.6 \times 10^{-19} \text{ C}$

$W = ?$

$W = QV$

$W = 1.6 \times 10^{-19} \times 3$

$W = 4.8 \times 10^{-19} \text{ J}$

7. $Q = ?$

$V = 12 \text{ V}$

$W = 4800 \text{ J}$

$W = QV$

$4800 = Q \times 12$

$Q = 400 \text{ C}$

8. $I = 5 \text{ A}$

$t = 10 \text{ minutes}$

$= 600 \text{ s}$

$Q = ?$

$Q = It$

$Q = 5 \times 600$

$Q = 3000 \text{ C}$

9. $t = ?$

$I = 25 \times 10^{-3} \text{ A}$

$Q = 96,500 \text{ C}$

$Q = It$

$96,500 = 25 \times 10^{-3} t$

$t = 3.86 \times 10^6 \text{ s}$

$= 6.4 \times 10^4 \text{ minutes}$

$= 1072 \text{ hours}$

$= 45 \text{ days}$

Unit 3 Electricity

3.2 Circuits

10. $Q = 240C$
 $t = 3 \text{ minutes}$
 $= 180s$
 $I = ?$

$$Q = It$$
$$240 = I \times 180$$
$$\underline{I = 1.3A}$$

11(a) $V = 24V$
 $I = 2.5A$
 $t = 20 \text{ minutes}$
 $= 1200s$
 $Q = ?$

$$Q = It$$
$$Q = 2.5 \times 1200$$
$$\underline{Q = 3000C}$$

(b) $W = QV$
 $W = 3000 \times 24$
 $\underline{W = 72,000J}$

(c) $P = IV$
 $P = 2.5 \times 24$
 $\underline{P = 60W}$

12(a) $I = 2.4A$
 $V = 12V$
 $W = 288 \times 10^3 J$
 $Q = ?$

$$W = QV$$
$$288 \times 10^3 = Q \times 12$$
$$\underline{Q = 24,000C}$$

(b) $Q = It$
 $24000 = 2.4t$
 $t = 10,000s$
 $\underline{= 1 \times 10^4 s}$

$$13(a) \quad R_T = R_1 + R_2$$

$$R_T = 12 + 20$$

$$\underline{R_T = 32 \Omega}$$

$$(b) \quad R_T = R_1 + R_2 + R_3$$

$$R_T = 12 + 8 + 16$$

$$\underline{R_T = 36 \Omega}$$

$$(c) \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{20} + \frac{1}{20}$$

$$\frac{1}{R_T} = \frac{2}{20}$$

$$\underline{R_T = 10 \Omega}$$

$$(d) \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{20} + \frac{1}{5}$$

$$\frac{1}{R_T} = 0.25$$

$$\underline{R_T = 4 \Omega}$$

Unit 3 Electricity
3.2 Circuits.

$$13e) \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{15}$$

$$\frac{1}{R_T} = 0.17$$

$$\underline{R_T = 6 \Omega}$$

$$f) \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{20} + \frac{1}{20} + \frac{1}{20}$$

$$\frac{1}{R_T} = \frac{3}{20}$$

$$\underline{R_T = 6.7 \Omega}$$

$$g) \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{20} + \frac{1}{5} + \frac{1}{4}$$

$$\frac{1}{R_T} = \frac{1}{2}$$

$$\underline{R_T = 2 \Omega}$$

$$h) \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{12} + \frac{1}{6} + \frac{1}{12}$$

$$\frac{1}{R_T} = 0.33$$

$$\underline{R_T = 3 \Omega}$$

$$(i) \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{40} + \frac{1}{10}$$

$$\begin{aligned} R_T &= R_1 + R_2 \\ &= 10 + 8 \\ &= \underline{18 \text{ k}\Omega} \end{aligned}$$

$$\frac{1}{R_T} = 0.125$$

$$R_T = 8 \text{ k}\Omega$$

Unit 3 Electricity
3.2 Circuits

13j)

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{48} + \frac{1}{16}$$

$$\frac{1}{R_T} = 0.083$$

R_T

$$R_T = 12 \Omega$$

$$R_T = R_1 + R_2 + R_3$$

$$R_T = 24 + 12 + 36$$

$$R_T = \underline{72 \Omega}$$

13k)

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{15} + \frac{1}{5}$$

$$\frac{1}{R_T} = 0.267$$

R_T

$$R_T = 3.75 \text{ k}\Omega$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{100} + \frac{1}{25}$$

$$\frac{1}{R_T} = 0.05$$

R_T

$$R_T = 20 \text{ k}\Omega$$

$$R_T = R_1 + R_2$$

$$R_T = 3.75 + 20$$

$$R_T = \underline{23.75 \text{ k}\Omega}$$

$$l) \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{12} + \frac{1}{36}$$

$$\frac{1}{R_T} = 0.111$$

$$\underline{R_T = 9 \Omega}$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{15} + \frac{1}{10} + \frac{1}{12}$$

$$\frac{1}{R_T} = 0.25$$

$$\underline{R_T = 4 \Omega}$$

$$R_T = R_1 + R_2$$

$$R_T = 9 + 4$$

$$\underline{R_T = 13 \Omega}$$

$$m) R_T = R_1 + R_2$$

$$= 24 + 12$$

$$= 36 \Omega$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{36} + \frac{1}{9}$$

$$\frac{1}{R_T} = 0.139$$

$$\underline{R_T = 7.2 \Omega}$$

Unit 3 Electricity

3.2 Circuits

13n)

$$\begin{aligned}R_T &= R_1 + R_2 \\ &= 100 + 400 \\ &= 500 \Omega\end{aligned}$$

$$\begin{aligned}R_T &= R_1 + R_2 \\ &= 200 + 300 \\ &= 500 \Omega.\end{aligned}$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{500} + \frac{1}{500} + \frac{1}{500}$$

$$\frac{1}{R_T} = 6 \times 10^{-3}$$

$$\underline{R_T = 167 \Omega}$$

14a)

$$\begin{aligned}R_T &= R_1 + R_2 \\ &= 16 + 8 \\ &= \underline{24 \Omega}\end{aligned}$$

b)

$$R = 24 \Omega$$

$$V = 12 \text{ V}$$

$$I = ?$$

$$I = \frac{V}{R}$$

$$I = \frac{12}{24}$$

$$\underline{I = 0.5 \text{ A}}$$

c)

$$\underline{16 \Omega}$$

$$\underline{8 \Omega}$$

$$V = IR$$

$$V = 0.5 \times 16$$

$$\underline{V = 8 \text{ V}}$$

$$V = IR$$

$$V = 0.5 \times 8$$

$$\underline{V = 4 \text{ V}}$$

15. $V = 6V$

$$R = 10 \times 10^3 \Omega$$

$$I = \frac{V}{R}$$

$$= \frac{5.5}{10 \times 10^3}$$

$$V_R = V_{\text{supply}} - V_{\text{thermistor}}$$

$$= 6 - 0.5$$

$$= 5.5V$$

$$= 5.5 \times 10^{-4} A$$

$$R_{\text{therm}} = \frac{V_{\text{therm}}}{I}$$

$$= \frac{0.5}{5.5 \times 10^{-4}}$$

$$= 909 \Omega$$

$$= \underline{909 \Omega}$$

16. $I = 0.2A$

$$V = IR$$

(a) $R_T = 20 + 30$

$$V = 0.2 \times 50$$

$$= 50 \Omega$$

$$V = \underline{10V}$$

$$\text{Emf} = ?$$

(b) $V = IR$

$$= 0.2 \times 20$$

$$= \underline{4V}$$

Unit 3 Electricity
3.2 Circuits

17. $P = IV$
 $24 = I \cdot 6$
 $I = 4A$

Voltage across resistor = $12 - 6 = 6V$

$$V = IR$$
$$6 = 4R$$
$$R = 1.5\Omega$$

18(a) $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$

$$\frac{1}{R_T} = \frac{1}{12} + \frac{1}{4}$$

$$\frac{1}{R_T} = 0.33$$

$$\underline{R_T = 3\Omega}$$

(b) $I = \frac{V}{R}$

$$I = \frac{24}{3}$$

$$\underline{I = 8A}$$

$$(c) \quad I = \frac{V}{R}$$

$$I = \frac{24}{12}$$

$$\underline{I = 2A}$$

$$I = \frac{V}{R}$$

$$I = \frac{24}{4}$$

$$\underline{I = 6A}$$

$$19(a) \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{40} + \frac{1}{10}$$

$$\frac{1}{R_T} = 0.125$$

$$R_T = 8\Omega$$

$$R_T = R_1 + R_2$$

$$R_T = 16 + 8$$

$$\underline{R_T = 24\Omega}$$

$$(b) \quad I = \frac{V}{R}$$

$$I = \frac{12}{24}$$

$$\underline{I = 0.5A}$$

$$c) \quad R_1 \quad V = IR$$

$$V = 0.5 \times 16$$

$$V = 8V$$

$$12 - 8 = 4V$$

$$\underline{\text{Voltage across } R_2 \text{ \& } R_3 = 4V}$$

$$(d) \quad R_2 \quad I = \frac{V}{R}$$

$$I = \frac{4}{40}$$

$$\underline{I = 0.1A}$$

$$R_3 : \quad I = \frac{V}{R}$$

$$I = \frac{4}{10}$$

$$\underline{I = 0.4A}$$

Unit 3 Electricity

3.2 Circuits

$$20. \quad \frac{1}{R_T} = \frac{1}{20} + \frac{1}{30}$$

$$\frac{1}{R_T} = 0.083$$

$$R_T = 12 \Omega$$

$$R_T = 24 + 12 + 36 = 72 \Omega$$

$$I_{\text{TOTAL}} = \frac{V}{R}$$

$$= \frac{18}{72}$$

$$= 0.25 \text{ A}$$

$$\begin{aligned} V_{\text{across } 24 \Omega} &= IR \\ &= 0.25 \times 24 \\ &= 6 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{\text{across } 36 \Omega} &= IR \\ &= 0.25 \times 36 \\ &= 9 \text{ V} \end{aligned}$$

$$V_{\text{parallel}} = 18 - 6 - 9 = 3 \text{ V}$$

$$\begin{aligned} I &= \frac{V}{R} \\ &= \frac{3}{20} \end{aligned}$$

$$= 0.15 \text{ A}$$

$$\begin{aligned} I &= \frac{V}{R} \\ &= \frac{3}{30} \end{aligned}$$

$$= 0.1 \text{ A}$$

$$I \text{ through } 24 \Omega = 0.25 \text{ A}$$

$$I \text{ through } 36 \Omega = 0.25 \text{ A}$$

$$I \text{ through } 20 \Omega = 0.15 \text{ A}$$

$$I \text{ through } 30 \Omega = 0.1 \text{ A}$$

$$21) \quad \frac{1}{R_T} = \frac{1}{3.3} + \frac{1}{4.7}$$

$$\frac{1}{R_T} = 0.516$$

R_T

$$R_T = 1.9 \text{ k}\Omega$$

$$R_T = 2.2 + 1.9 = 4.1 \text{ k}\Omega$$

$$I = \frac{V}{R}$$

$$I = \frac{1.5}{4.1 \times 10^3}$$

$$I = 3.7 \times 10^{-4} \text{ A} \quad (\text{Reading on Ammeter - total current})$$

Voltage across $2.2 \text{ k}\Omega$: $V = IR$

$$V = 3.7 \times 10^{-4} \times 2200$$
$$V = 0.8 \text{ V}$$

Voltage of Parallel component: $1.5 - 0.8 = 0.7 \text{ V}$

Ammeter ($3.3 \text{ k}\Omega$): $I = \frac{V}{R}$

$$I = \frac{0.7}{3300}$$

$$I = 2.1 \times 10^{-4} \text{ A}$$

$$I = 2.1 \times 10^{-4} \text{ A}$$

Ammeter ($4.7 \text{ k}\Omega$): $I = \frac{V}{R}$

$$I = \frac{0.7}{4700}$$

$$I = 1.5 \times 10^{-4} \text{ A}$$

$$I = 1.5 \times 10^{-4} \text{ A}$$

Unit 3: Electricity

3.2 Circuits

$$22. \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{15} + \frac{1}{10}$$

$$\frac{1}{R_T} = 0.17$$

$$R_T = 6 \Omega$$

$$R_T = \frac{V}{I}$$

$$R_T = \frac{9}{0.25}$$

$$R_T = 36 \Omega$$

$$\underline{R = 36 - 6 = 30 \Omega}$$

23(a) use ratio: $12:4$
 $3:1$

$$3 \times 2 = 6$$

therefore 6A flows through 4Ω .

(b) current in $6\Omega = 6 + 2 = 8A$.

(c)
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{12} + \frac{1}{4}$$

$$\frac{1}{R_T} = 0.33$$

$$R_T = 3\Omega.$$

$$\begin{aligned} V &= IR \\ &= 8 \times 9 \\ &= \underline{72V} \end{aligned}$$

24(a)
$$\frac{V_1}{V_2} = \frac{R_1}{R_2}$$

$$\frac{4}{8} = \frac{R}{250}$$

$$R = \frac{4 \times 250}{8}$$

$$\underline{R = 125\Omega.}$$

Unit 3 Electricity
3.2 Circuits

$$24(b) \quad \frac{V_1}{V_2} = \frac{R_1}{R_2}$$

$$\frac{5}{19} = \frac{3.3}{R}$$

$$R = \frac{3.3 \times 19}{5}$$

$$\underline{R = 12.5 \text{ k}\Omega}$$

$$25(a) \quad V_1 = \left(\frac{R_1}{R_1 + R_2} \right) V_s$$

$$V_1 = \frac{10}{10 + 15} \cdot 5$$

$$\underline{V_1 = 2 \text{ V}}$$

$$(b) \quad V_1 = \frac{R_1}{R_1 + R_2} \cdot V_s$$

$$V_1 = \frac{470}{470 + 330} \cdot 12$$

$$\underline{V_1 = 7 \text{ V}}$$

$$(c) \quad V_1 = \left(\frac{R_1}{R_1 + R_2} \right) V_s$$

$$V_1 = \left(\frac{1000}{1000 + 100} \right) 5$$

$$\underline{V_1 = 4.5 \text{ V}}$$

$$(d) \quad V_1 = \left(\frac{R_1}{R_1 + R_2} \right) V_s$$

$$V_1 = \left(\frac{10000}{10 \times 10^3 + 1.2 \times 10^6} \right) 5$$

$$\underline{V_1 = 0.04 \text{ V}}$$

$$25(e) \quad V_1 = \left(\frac{R_1}{R_1 + R_2} \right) V_s$$

$$V_1 = \left(\frac{5}{5 + 15} \right) 5$$

$$V_1 = 1.25V$$

$$(f) \quad \frac{1}{R_T} = \frac{1}{56} + \frac{1}{22}$$

$$V_1 = \left(\frac{R_1}{R_1 + R_2} \right) V_s$$

$$\frac{1}{R_T} = 0.06$$

$$V_1 = \left(\frac{15.8}{15.8 + 33} \right) 12$$

$$R_T = 15.8k\Omega$$

$$V_1 = \underline{3.9V}$$

$$(g) \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$V_1 = \left(\frac{R_1}{R_1 + R_2} \right) V_s$$

$$= \frac{1}{10} + \frac{1}{470}$$

$$V_1 = \left(\frac{9.8}{9.8 + 330} \right) 5$$

$$\frac{1}{R_T} = \frac{24}{235}$$

$$V_1 = \underline{0.14V}$$

$$R_T = 9.8\Omega$$

$$(h) \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$V_1 = \left(\frac{R_1}{R_1 + R_2} \right) V_s$$

$$\frac{1}{R_T} = \frac{1}{68} + \frac{1}{56}$$

$$V_1 = \left(\frac{47}{47 + 30.7} \right) 5$$

$$\frac{1}{R_T} = \frac{31}{952}$$

$$V_1 = \underline{3V}$$

$$R_T = 30.7k\Omega$$

Unit 3 Electricity

3.2 Circuits

Internal Resistance

27

$$(a) \quad I = \frac{E}{R+r}$$

$$I = \frac{12}{(7.5 + 0.5)}$$

$$\underline{I = 1.5A}$$

$$(b) \quad \begin{aligned} \text{t.p.d} &= IR \\ &= 1.5 \times 7.5 \\ &= \underline{11.25V} \end{aligned}$$

$$(c) \quad \underline{\text{'lost volts'} = 12 - 11.25 = 0.75V}$$

$$28a) \quad \begin{aligned} \text{t.p.d} &= IR \\ &= 6 \times 3 \\ &= \underline{18V} \end{aligned}$$

$$(b) \quad \begin{aligned} \text{'lost volts'} &= \text{Emf} - \text{t.p.d} \\ &= 24 - 18 \\ &= 6V \end{aligned}$$

$$\text{'lost volts'} = Ir$$

$$6 = 6r$$

$$\underline{r = 1\Omega}$$

29(a) $E = 1.5V$
 $r = 0.6\Omega$
 $R = 3.3\Omega$
 $I = ?$

$$I = \frac{E}{R+r}$$

$$I = \frac{1.5}{(3.3+0.6)}$$

$$\underline{I = 0.38A}$$

(b) t.p.d = IR
 $= 0.38 \times 3.3$
 $= \underline{1.27V}$

(c) short circuit: $I = \frac{E}{r}$
 $I = \frac{1.5}{0.6}$
 $\underline{I = 2.5A}$

30 $E = 12.4V$
 $r = 0.06\Omega$
 $I_s = ?$

$$I_s = \frac{E}{r}$$

$$I_s = \frac{12.4}{0.06}$$

$$\underline{I_s = 207A}$$

31 $E = 6V$
 $I = 24A$
 $r = ?$

$$r = \frac{E}{I}$$

$$r = \frac{6}{24}$$

$$\underline{r = 0.25\Omega}$$

Unit 3: Electricity
3.2 Circuits

3.2 $E = 15V$
 $r = 0.5\Omega$
 $R = 4.5\Omega$

(a) $I = \frac{E}{R+r}$

$I = \frac{15}{4.5 + 0.5}$
 $I = 0.3A$

$P = I^2 R$
 $= 0.3^2 \times 4.5$
 $= 0.405W$

(b) $P = I^2 R$
 $= 0.3^2 \times 5$
 $= 0.045W$

33 $E = 1.6V$
 $r = 0.25\Omega$
 $I = 2.4A$

$E = IR + Ir$
 $1.6 = 2.4R + (2.4 \times 0.25)$
 $1.6 = 2.4R + 0.6$
 $2.4R = 1$
 $R = 0.4\Omega$

t.p.d. = IR
 $= 2.4 \times 0.4$
 $= 1V$

34.

$$E = 12V$$

$$E.p.d = 10.5V$$

$$R = 2.8\Omega$$

$$r = ?$$

$$E.p.d = IR$$

$$10.5 = I \times 2.8$$

$$I = 3.75A$$

$$\begin{aligned} \text{'lost volts'} &= 12 - 10.5 \\ &= 1.5V \end{aligned}$$

$$\begin{aligned} \text{'lost volts'} &= Ir \\ 1.5 &= 3.75r \\ \underline{r} &= \underline{0.4\Omega} \end{aligned}$$

35.

$$E = 1.53V$$

$$E.p.d = 1.32V$$

$$I = 0.42A$$

$$r = ?$$

$$\begin{aligned} \text{'lost volts'} &= 1.53 - 1.32 \\ &= \underline{0.21V} \end{aligned}$$

$$r = \frac{\text{'lost Volts'}}{I}$$


$$r = \frac{0.21}{0.42}$$

$$\underline{r = 0.5\Omega}$$

36. a + b = see graph.

$$(c) \quad I = \frac{E}{r} = \frac{3}{1.5} = 2A$$

Question 36: Voltage against Current

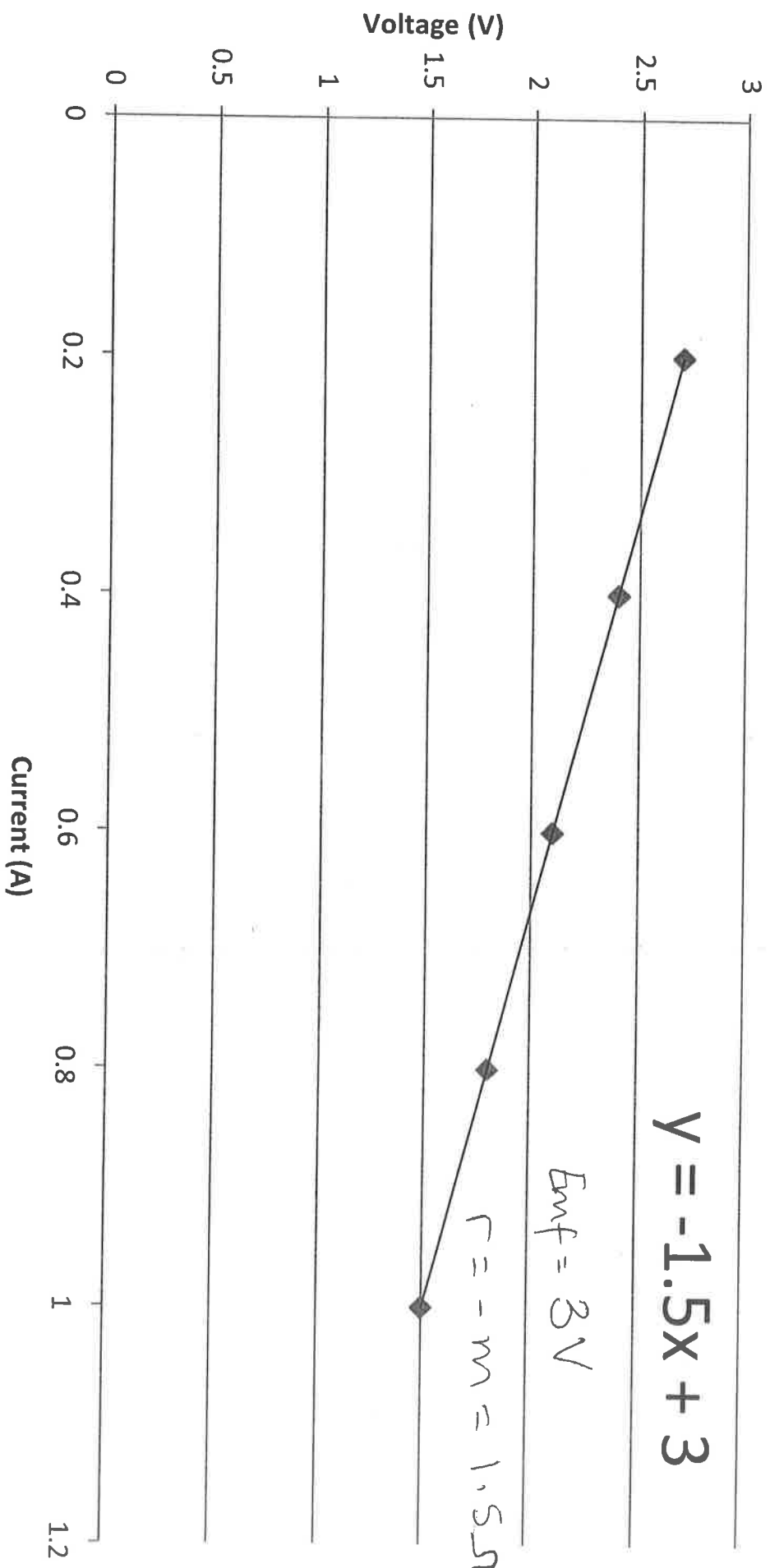

Unit 3 Electricity
3.2 Circuits

37. When the switch is closed the overall load resistance will decrease.
This will lead to an increase in the current.
since E & r are constant in the equation:

$$E = IR + Ir$$

Ir (the lost volts) must increase which in turn means IR (the t.p.d) must decrease. Since the t.p.d is lower the lamp will get dimmer.

38. $E = 9V$
 $r = 2\Omega$

$$I = \frac{V}{R}$$

$$I = \frac{5}{16}$$

$$I = 0.31A$$

$$\begin{aligned} \text{'lost volts'} &= Ir \\ &= 0.31 \times 2 \\ &= 0.62V \end{aligned}$$

$$\text{Emf} = \text{t.p.d} + \text{'lost volts'}$$

therefore, $\text{t.p.d} = 9 - 0.62$
 $= 8.38V$

$$\begin{aligned} V_R &= 8.38V \\ I &= 0.31A \\ R &= ? \end{aligned}$$

$$\begin{aligned} R &= \frac{V}{I} = \frac{8.38}{0.31} \\ &= \underline{\underline{11\Omega}} \end{aligned}$$

39(a)

(i) $E = 6V$

$R = 1.5\Omega$

$I = 3A$

t.p.d = IR

$= 1.5 \times 3$

$= 4.5V$

'lost volts' = $6 - 4.5$
 $= 1.5V$

(ii)

'lost volts' = Ir

$1.5 = 3r$

$r = 0.5\Omega$

(b) If R increases the current will decrease. The Emf (E) of the cell is fixed as is the internal resistance (r). This means that the lost volts will decrease as $E = IR + Ir$ with ' Ir ' representing the 'lost volts'.