



James Clerk Maxwell - the Scottish physicist - famously developed the theory on electromagnetic radiation.





An electromagnet lifting scrap.



The Transrapid maglev train uses electromagnetic suspension to lift itself above the track.

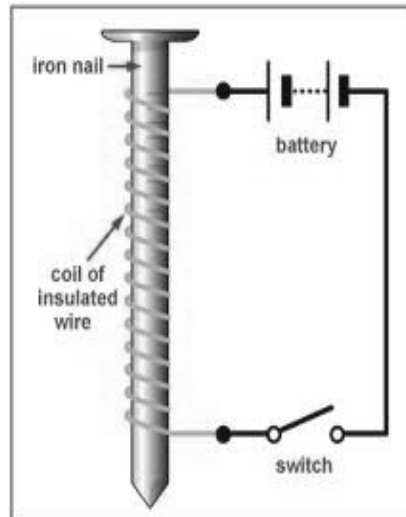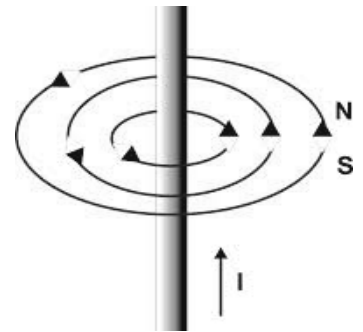
### Electromagnetism

When a current passes through a wire, a magnetic field is produced. By wrapping a wire round a soft iron core an electromagnet is produced. The more wires that are wound together the greater the strength of the electromagnet. When the current is switched off, the magnetic field fails.



A simple electromagnet, like the one to the left, is easy to make and can be used to demonstrate the on-off mechanism which is put to use in many ways. Typical uses of this effect are the bell and the relay.

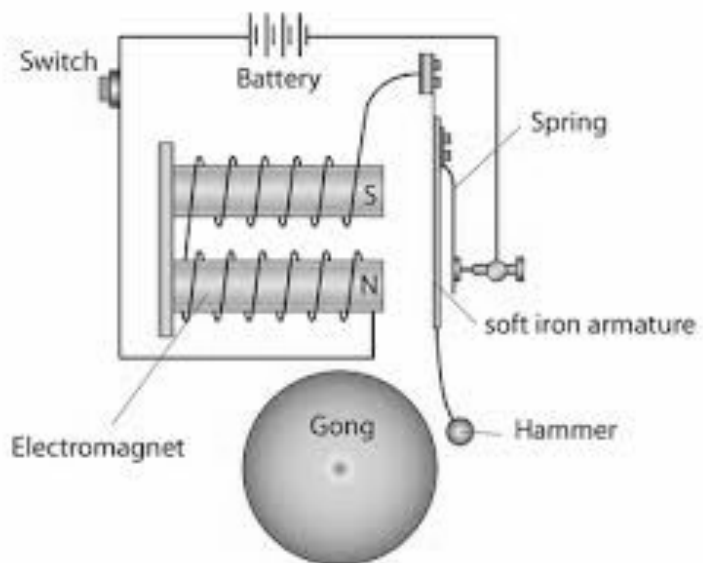In the bell the clapper is pulled towards the gong by the electromagnet but this causes a break in the circuit and the electromagnet fails. The spring attached to the clapper makes the clapper return to its original position and the whole action starts again.




A relay is an electromagnetic switch which can be used to operate a high current circuit.


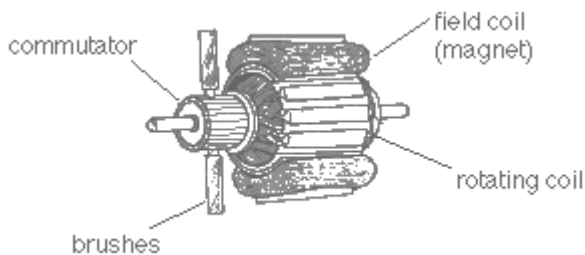
### The Electric Motor

When a wire carrying a current is placed between the poles of a magnet then the wire has a force acting on it. The direction of the force can be changed by reversing either the current or the direction of the magnetic field.



In an electric motor, coils of wire are placed between the poles of a magnet and, as a current flows in the wires, the coils will rotate. The coils will keep on rotating because of the **commutator**. This is a ring split into two which reverses the direction of current. Current is fed in to the coils by the **brushes**.



### Induced Voltage

If a conductor cuts across the lines of a magnetic field, then a voltage will be induced across the ends of a conductor. Note the magnet can move with the conductor stationary or vice versa. An induced voltage will be produced provided the conductor experiences a **changing magnetic field**.

Magnets with opposite poles facing.

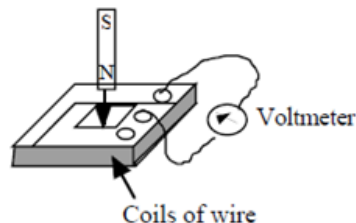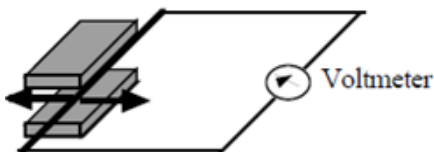


The size of the induced voltage depends on -


- the magnetic field strength
- the number of coils
- the speed of the motion

This is the foundations of electricity generation.

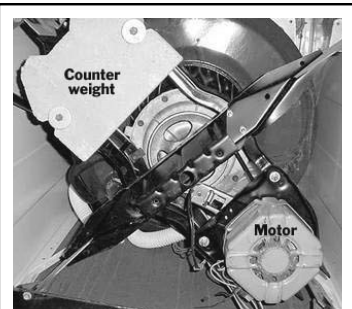
In S1, you looked at a dynamo which is a simple generator. Generators change kinetic energy into electrical energy. They do the opposite of electric motors.



Inside of a washing machine.

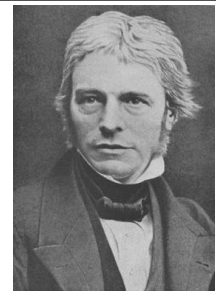

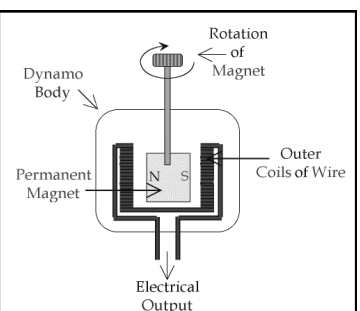Michael Faraday who built the first electric motor around 1830.




A simple diagram of a dynamo.





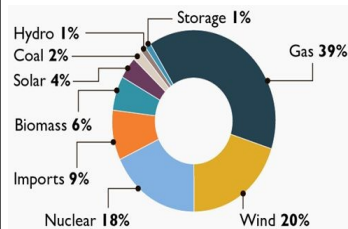A bicycle dynamo can power a mobile phone.




We are closing down coal power stations in the UK. We had our first coal free month in May 2020.



Do you know who invented the lightbulb?

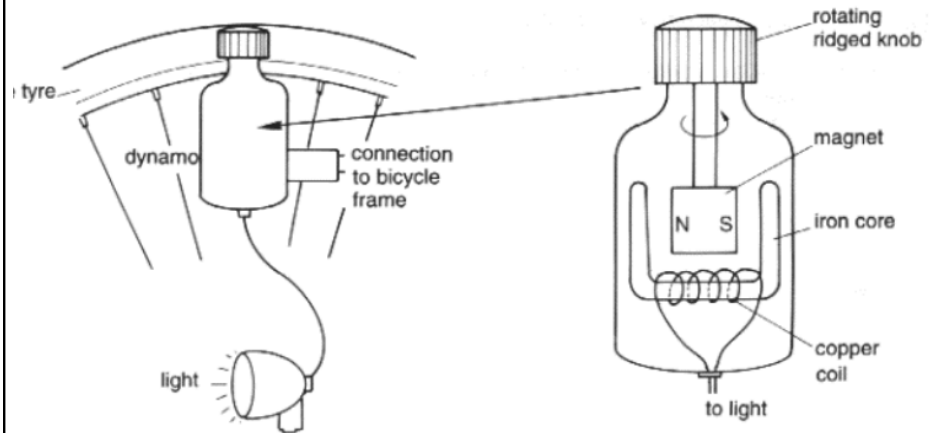A bicycle dynamo is a small electrical generator. The magnet rotates inside a coil of wire and electrical energy is produced. This electrical energy is changed to light in the lamp.




### Generation of Electricity

On a larger scale, electricity is generated in power stations in a similar way. Generators in power stations (thermal, nuclear or hydroelectric) rely upon the relationship between electricity and magnetism in order to produce electrical energy.
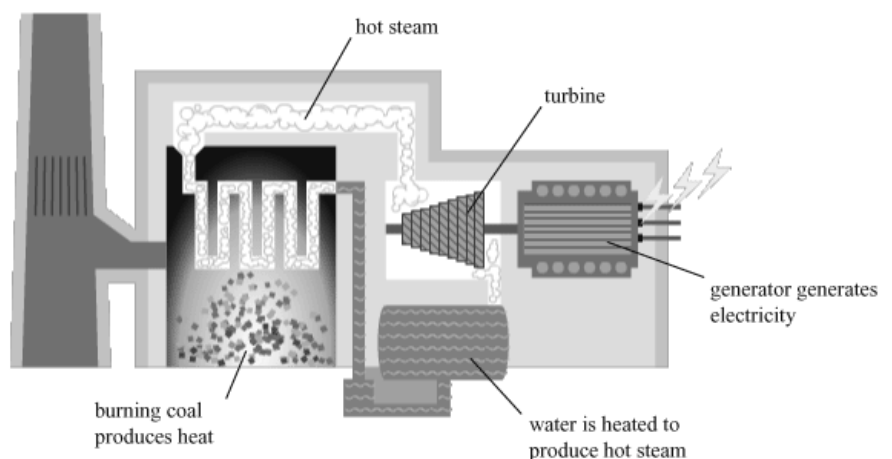
#### Thermal Stations

Thermal power stations generate electricity by burning fossil fuels. Oil or coal is burned to produce heat, which turns water into steam. The steam then travels at high pressure and turns a turbine which turns a generator which converts kinetic energy into electrical energy.




The burning of fossil fuels produces  $\text{CO}_2$  which can contribute to global warming. Fossil fuels will also run out eventually and so we have to find alternative methods for generating electricity.



## S2 Electricity

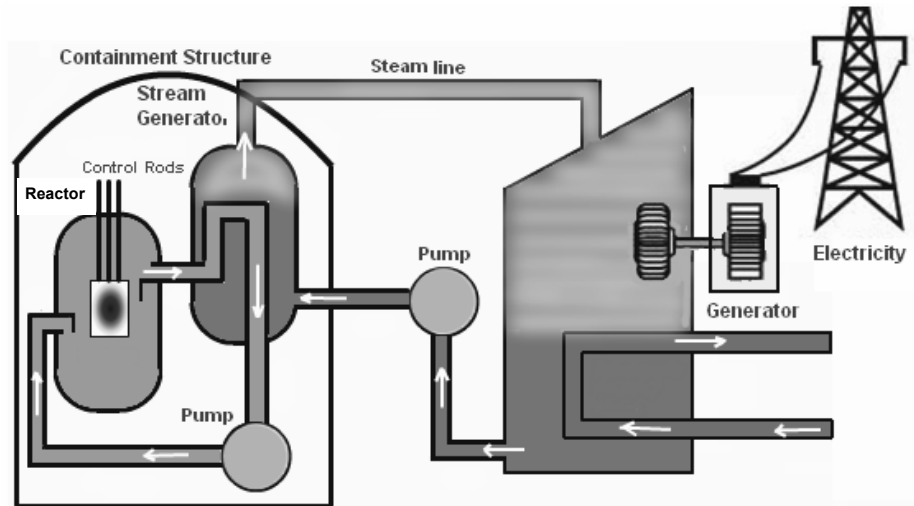
### Nuclear Power Stations

In a nuclear power station heat is created in a nuclear reactor. This heat changes water into steam which turns a turbine. The turbine, again, turns a generator which converts kinetic energy into electrical energy.



Nuclear power stations do not produce gases which contribute to global warming, but they produce radioactive waste which is harmful to humans and other living things.

### Hydroelectric Power Stations

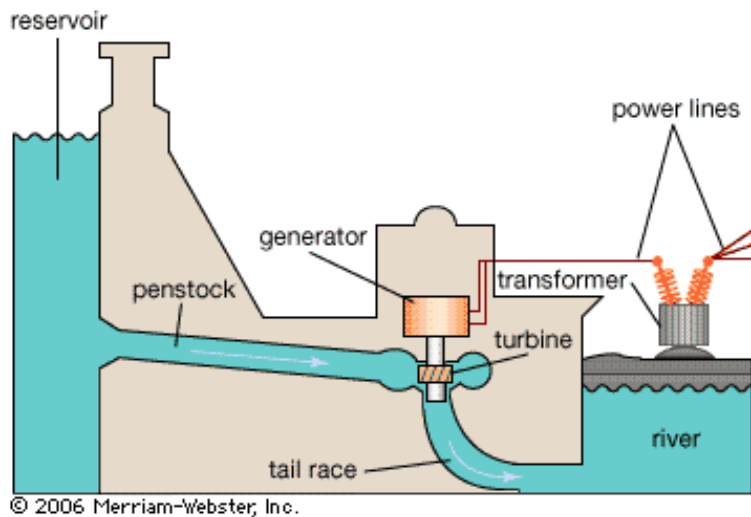

Hydroelectric power uses the potential energy of water stored in dams to turn dynamos and make electricity.

Hydroelectric energy is renewable- as long as it rains the dam will refill.

### Wind Turbines


Wind turbines harness the kinetic energy of the wind and turn it into electrical energy via a generator.



Nuclear fuel — Uranium




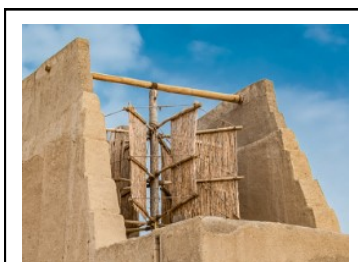Cruachan Hydro Power Plant. Why is Scotland suited to hydroelectric power stations?



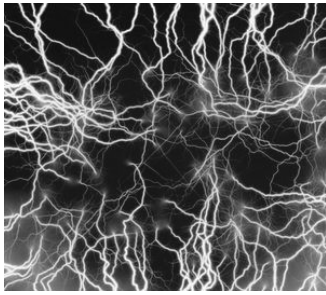Wind energy was first developed in 200 BC in Persia and China.






Static Charge



Van de Graaf fun.

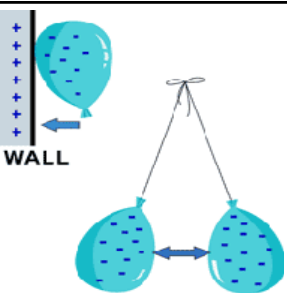


Balloons and static electricity.

## Charge

With your teacher you used a Van de Graaf generator, a machine which rubs a rubber belt over a plastic roller. When the belt is **rubbed** it gets an electric charge, which it passes to the dome. This static charge can create sparks.

You found out that there are two types of electrical charge, **positive and negative**.

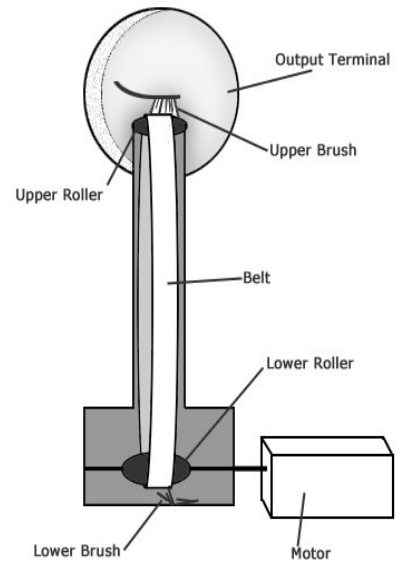Electricity is a **flow of tiny, negatively charged particles called electrons**. Electrons are much smaller than atoms.




You also carried out experiments in which pieces of plastic were rubbed to give an electrical charge.

**Any material can be given an electric charge by rubbing.**


When plastic rods which both had positive charges were brought close to each other the rods moved away - they repelled.

Positive is repelled by positive.  
Negative is repelled by negative.

We say that **like charges repel**.

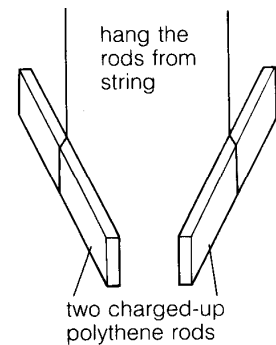

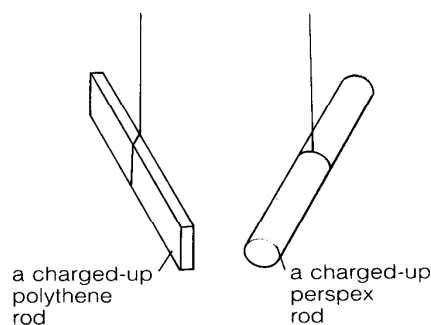When a positively charged rod is brought close to a negatively charged rod they attract. Positive charges are the opposite of negative charges.



We say that **opposite charges attract**.

Balloons can be given an electric charge by rubbing. The picture opposite shows that **like charges repel** and **opposite charges attract**.




### Electrical Circuits

#### Conductors and Insulators

**A conductor is a substance which lets electricity flow through it easily.**

Metals are good conductors of electricity. Graphite - the "lead" in pencils is a non metal which conducts electricity.

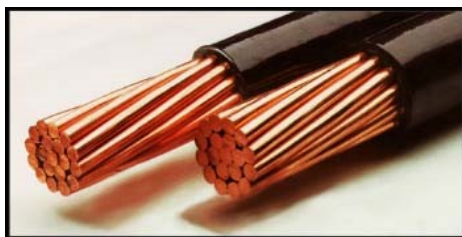
**An insulator is a substance which does not let electricity flow through it easily.**




Metals are used at the centre of wires to conduct electricity and plastic is used to insulate the wires.
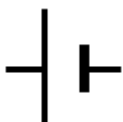
#### Electrical Symbols

**Each electrical component is represented by a symbol, which is easy to draw.** The symbols are used to draw electrical circuits. All scientists in the world- no matter their language have agreed to use the same symbols.




Cell

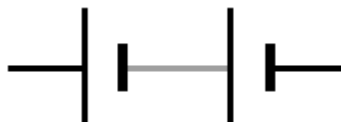

Battery




Lamp

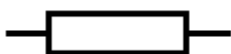

Resistor



Voltmeter

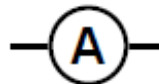

Ammeter



Switch



The wires attached to pylons are made of aluminium and iron which are conductors.



Light bulbs are not efficient - most of the electrical energy changes into heat energy.



Multi-meters can be used as voltmeters, ammeters and ohmmeters.





The Amp is named after the famous scientist - Andre Ampere.



Batteries change chemical energy into electrical energy.




The Volt is named after another famous Scientist, Allesandro Volta.

### Current

**Current is the flow of charges (electrons) around a circuit.**

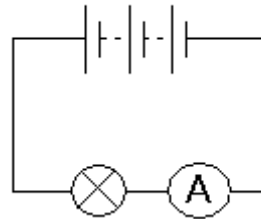**Current is measured in amps - short for Amperes. The symbol for amps is A.**

Current is measured with an ammeter, **to measure current the ammeter is placed in the circuit along side the component.**



The ammeter in the circuit, above, is measuring the current flowing through the bulb.

### Voltage


Batteries provide electrons with the energy to move. The push a battery gives to electrons is called the voltage of the battery.

**Voltage is a measure of the energy given to the charge (electrons) in a circuit.**

When batteries are joined together the voltages can add or cancel depending on the way the batteries are joined.

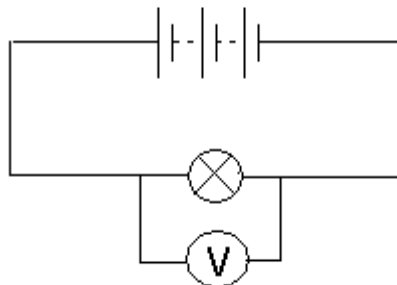**Voltage is measured in Volts. The symbol for volts is V.**

Voltage is measured with a voltmeter, **to measure the voltage across a component the voltmeter is placed across the component.**



The voltmeter in the circuit, above, is measuring the voltage across the bulb.




### Resistance

Materials oppose current and some materials oppose it more than others. This opposition to current is called resistance. Every material has an electrical resistance. **The greater the resistance, the smaller the current that flows.**

Every electrical component has resistance. Components called resistors are used to provide resistance in circuits. **Resistors cause electrical energy to be changed to heat energy.**

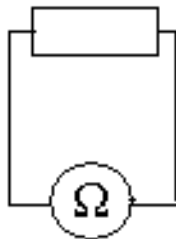**Resistance is measured in ohms. The Greek letter omega ( $\Omega$ ) is the symbol for ohms.**

Resistance can be measured with an ohmmeter. To measure resistance, connect the ohmmeter directly across the resistor or component.




### Variable Resistors


Variable resistors are resistors in which the resistance can be changed. This can be done by altering the length of wire in the variable resistor. The longer the wire, the greater the resistance. Variable resistors are used to control the current flowing in a circuit.

Variable resistors have many uses. They are used in volume or brightness controls on televisions, dimmer switches on lights, thermostats etc.

The symbol for a variable resistor is

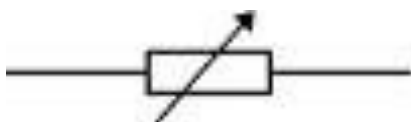

Georg Ohm,  
the German physicist.

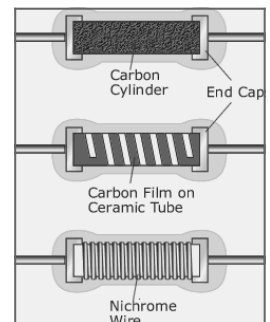


Inside a resistor.



Inside a variable resistor.



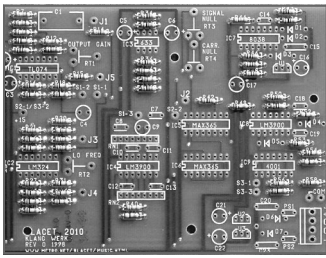

Resistors on a printed circuit board.




Defibrillators give an electric shock to the heart to restore a stable rhythm.



An average lightning strike discharges about 30,000 amperes.
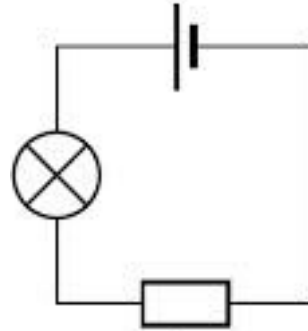
## Series Circuits


A series circuit is a circuit in which the components are connected one after the other, in series. There is only one path for the current to follow. Any break in the circuit will stop the flow of charge and cause the whole circuit to stop working.



A series circuit with a cell, a lamp and a resistor.

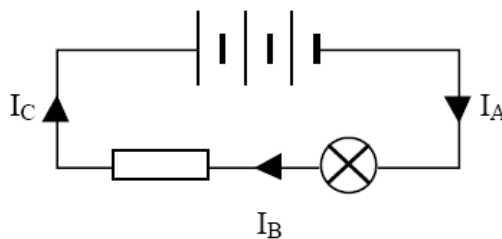
## Current and Voltage in Series Circuits

The current is the same at all points in a series circuit because there is **only one** path for the current to flow.



$$I_A = I_B = I_C$$

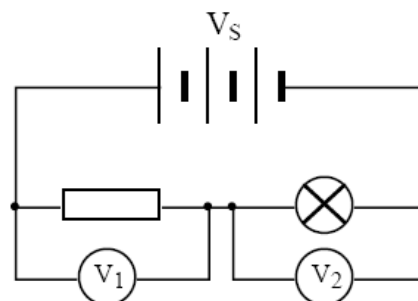The sum of the voltages across the components in a series circuit is equal to the voltage of the supply.




$$V_s = V_1 + V_2$$



## S2 Electricity
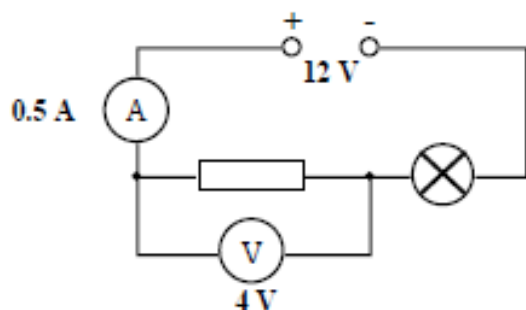
### Example

In the circuit below the ammeter reading is 0.5 A and the voltmeter reading is 4 V.



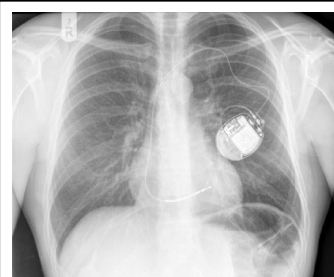
- (a) What is the current through the lamp?
  - (b) What is the potential difference across the lamp?
- 
- (a) *The current through the lamp is 0.5 A as the current is the same at all points in a series circuit.*
  - (b) *Voltage across lamp = Supply voltage - voltage across resistor  
= 12 - 4  
= 8 V*



Sharks detect electric fields given off by potential meals.



Power lines carry electricity at 400,000 volts



An artificial pacemaker sends electric pulses through wires to a patient's heart .






Christmas tree lights...  
series or parallel ?



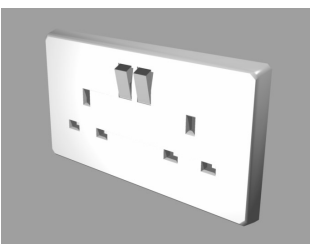
Cars have many  
parallel circuits to  
ensure that all the  
electrical parts work.



Sockets in a house-  
hold are arranged in  
special parallel circuits  
called ring circuits.
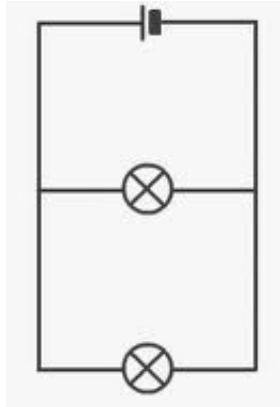
## Parallel Circuits


A parallel circuit is a circuit which has more than one path (branch) for the current to follow. A break in one of these paths will not prevent other paths from carrying charge. They are called 'parallel' circuits because on a circuit diagram, the different branches of the circuit run parallel to each other.



A parallel circuit with a cell and two  
bulbs. Each component is on a  
different branch.
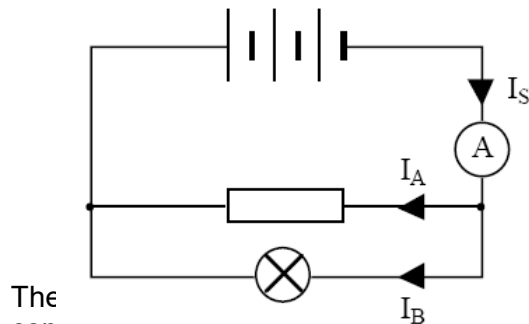
## Current and Voltage in Parallel Circuits


In a parallel circuit the current has **more than one** path to follow. This means that the supply current splits through each parallel branch.



$$I_s = I_A + I_B$$

The  
con

nts is the same for all

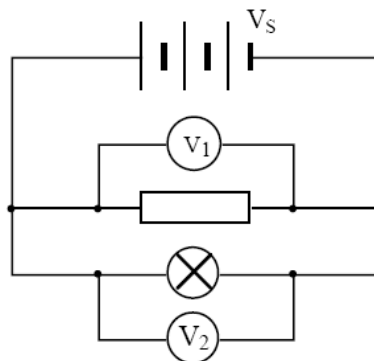


$$V_s = V_1 = V_2$$



## S2 Electricity
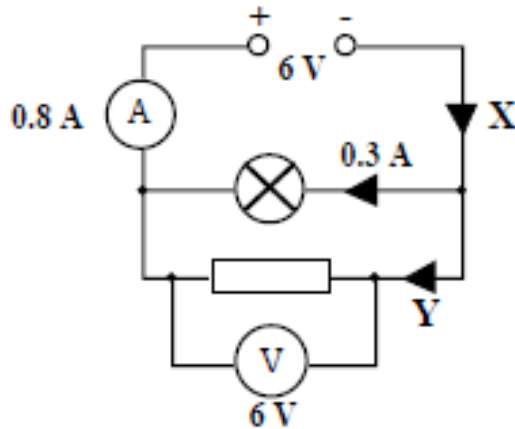
### Example



In the parallel circuit below the ammeter reads 0.8 A, the current through the lamp is 0.3 A and the voltmeter reads 6 V.



- (a) What is the voltage across the lamp?
- (b) What are the current values at X and Y?

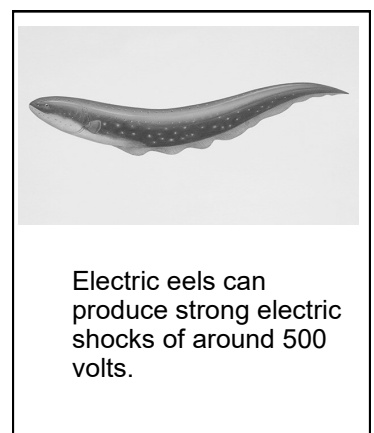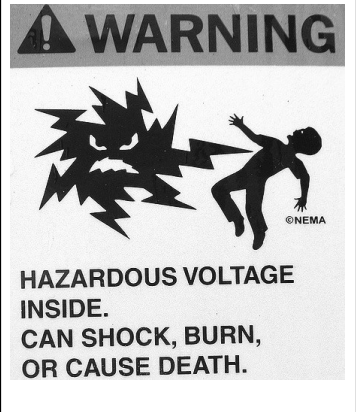- (a) *The voltage across the lamp is 6 V as the voltage across each branch in a parallel circuit is the same.*
- (b) *The current at X is 0.8 A as it is the supply current (it has not split between the branches yet).*

*The current at Y is  $0.8 - 0.3 = 0.5$  A  
(as the supply current of 0.8 A is split between the branches).*





Electricity from the mains can flow through our bodies.




Switches control the flow of electricity.



Electricity meters measure the amount of electricity used.
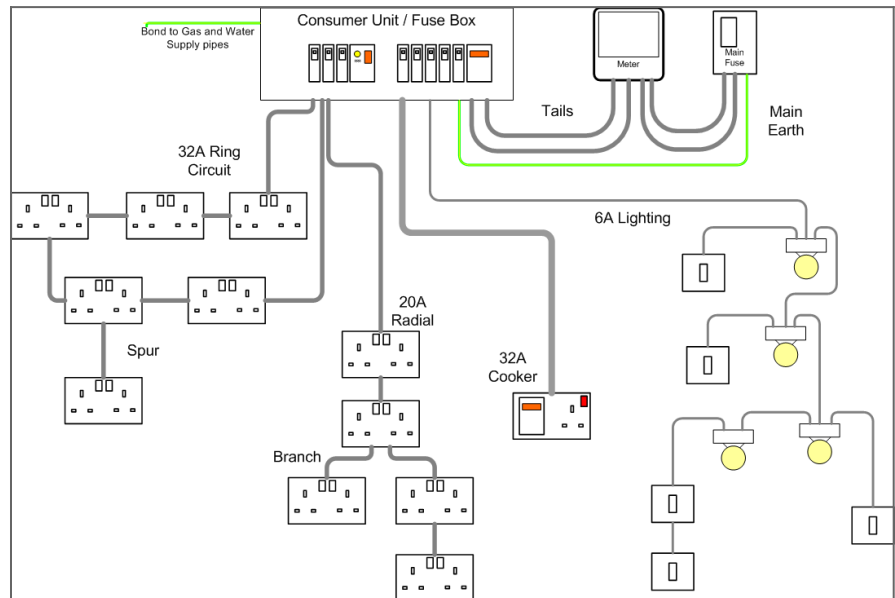
### Household Electricity


Electricity supplied to houses is called mains electricity. Every electrical appliance in your house is connected to the mains electricity by wires and a plug. All appliances in Britain are designed to operate at the mains voltage, **230 volts**.



To ensure that all the appliances receive this voltage **household circuits are connected in parallel**.
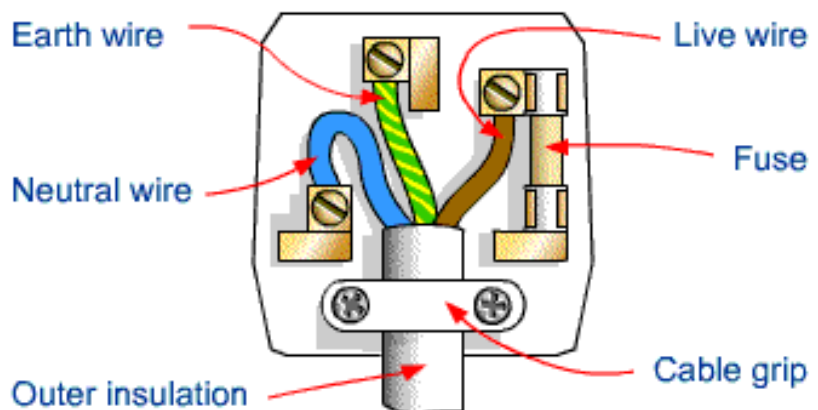
### The Plug

All appliances are connected to the mains by a plug, which must be wired correctly. It is dangerous to operate an appliance if the wires are not connected as shown below.




The **live wire is brown**, the **neutral wire is blue** and the **earth wire is green and yellow**. The live and neutral wires carry the current to the appliance. **The earth wire is a safety device**.


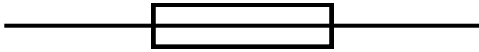
### The Fuse

The fuse in a plug is a safety device to protect the cable. It melts if the current in the cable gets too high. All plugs contain a fuse, which is next to the live pin and wire. The correct value of fuse must be used for the appliance connected to the plug to operate safely. The symbol for a fuse is shown below :



The two sizes of fuse recommended for use in the mains plugs are 3 A and 13 A. The power rating of an appliance is used to choose the correct fuse.

Electricity enters our homes through the consumer unit which contains mains fuses. Each circuit in the home is connected to an appropriate mains fuse in the unit which protects the wiring.




Modern consumer units contain circuit breakers. A circuit breaker is an automatic switch that can be used instead of a fuse. Circuit breakers react quickly to large currents and can be reset.

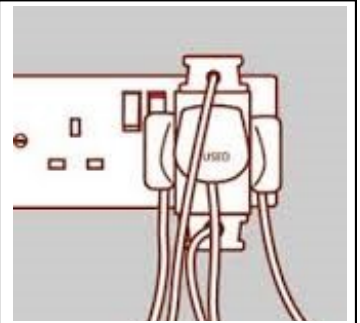
### Safety in the Home

Playing with electricity can be deadly. Carelessness can be dangerous, too. Despite this, many people get into bad habits when they use electricity.

Sockets should not be overloaded, frayed wires should not be used, appropriate fuses should be used and electrical appliances should not be used around water. **Moisture increases the conductivity of the human body.**



Too many plugs can overload a socket.

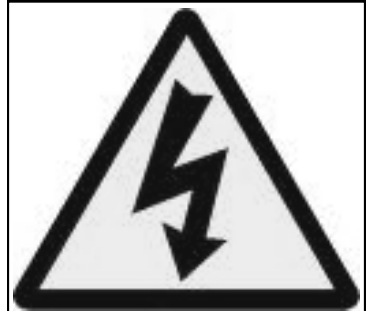

Watch out for the electrical hazard symbol.



Resistance in electrical cables can prove costly.



