
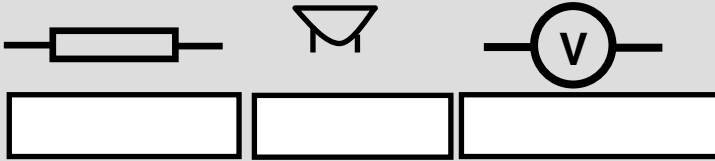


Homework – Electricity 1

1. Write down the name of an electrical device you could not live without. Why could you not live without this device?

2. Electricity likes to flow to the ground. What is static electricity?

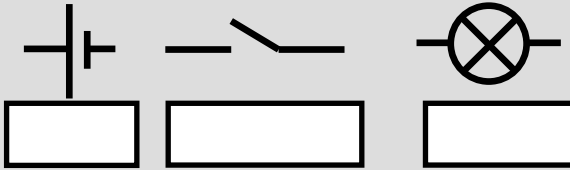3. What are these the electrical symbols for?




3. Draw a circuit diagram with a cell, bulb and switch in series.

Homework – Electricity 1

1. Write down the name of an electrical device you could not live without. Why could you not live without this device?

2. Electricity likes to flow to the ground. What is static electricity?

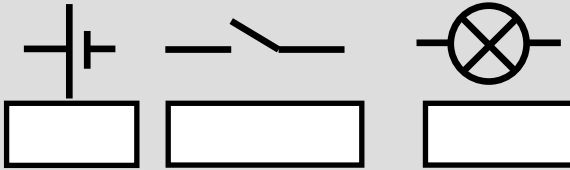3. What are these the electrical symbols for?





3. Draw a circuit diagram with a cell, bulb and switch in series.

Homework – Electricity 1

1. Write down the name of an electrical device you could not live without. Why could you not live without this device?

2. Electricity likes to flow to the ground. What is static electricity?

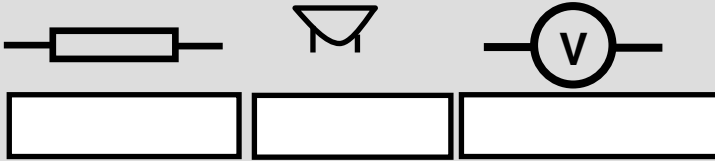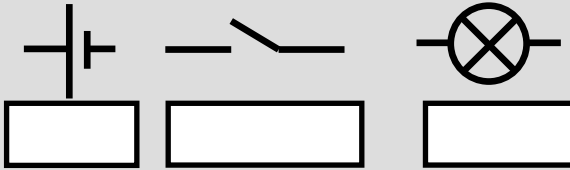3. What are these the electrical symbols for?





3. Draw a circuit diagram with a cell, bulb and switch in series.

Homework – Electricity 1

1. Write down the name of an electrical device you could not live without. Why could you not live without this device?

2. Electricity likes to flow to the ground. What is static electricity?

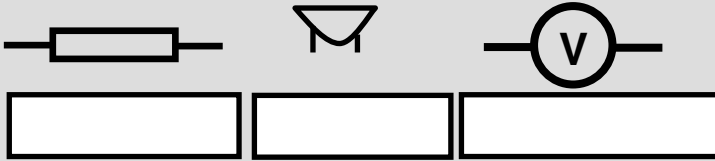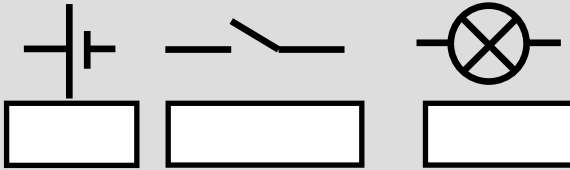3. What are these the electrical symbols for?




3. Draw a circuit diagram with a cell, bulb and switch in series.

Homework – Electricity 1

1. Write down the name of an electrical device you could not live without. Why could you not live without this device?

2. Electricity likes to flow to the ground. What is static electricity?

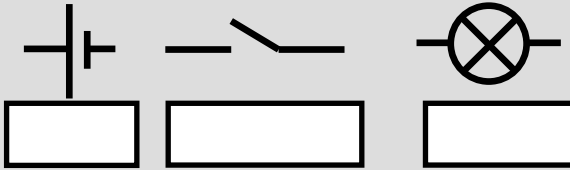3. What are these the electrical symbols for?




3. Draw a circuit diagram with a cell, bulb and switch in series.

Homework – Electricity 1

1. Write down the name of an electrical device you could not live without. Why could you not live without this device?

2. Electricity likes to flow to the ground. What is static electricity?

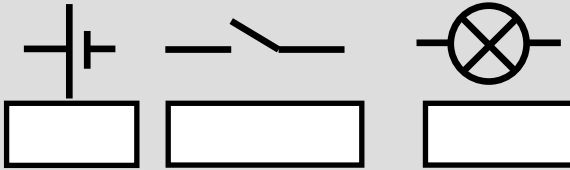3. What are these the electrical symbols for?




3. Draw a circuit diagram with a cell, bulb and switch in series.

Homework – Electricity 1

1. Write down the name of an electrical device you could not live without. Why could you not live without this device?

2. Electricity likes to flow to the ground. What is static electricity?

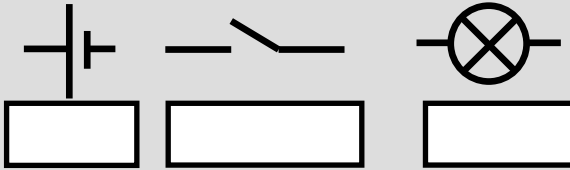3. What are these the electrical symbols for?





3. Draw a circuit diagram with a cell, bulb and switch in series.

Homework – Electricity 1

1. Write down the name of an electrical device you could not live without. Why could you not live without this device?

2. Electricity likes to flow to the ground. What is static electricity?

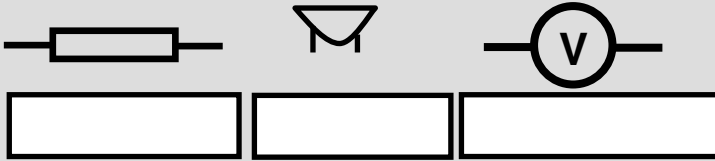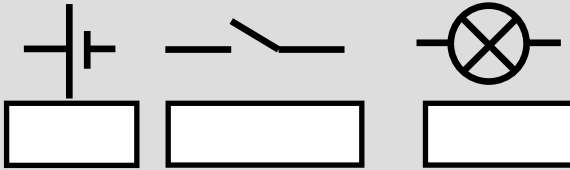3. What are these the electrical symbols for?





3. Draw a circuit diagram with a cell, bulb and switch in series.

Homework – Electricity 1

1. Write down the name of an electrical device you could not live without. Why could you not live without this device?

2. Electricity likes to flow to the ground. What is static electricity?

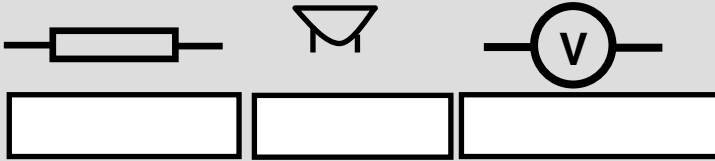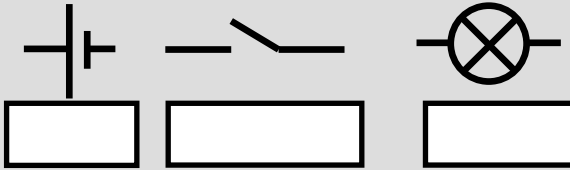3. What are these the electrical symbols for?



3. Draw a circuit diagram with a cell, bulb and switch in series.