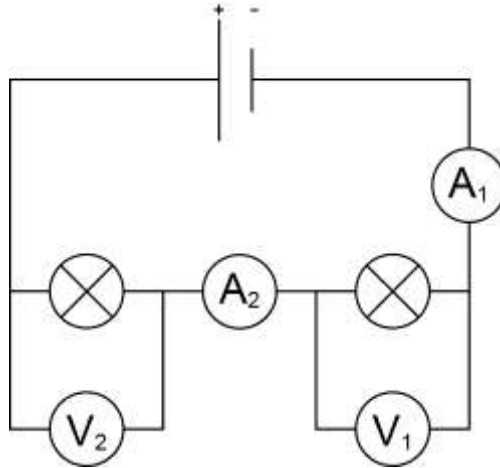


N5

## Complex Circuits with Current and Voltage

### Series Circuit



All bulbs are identical

- (a) V<sub>1</sub> reads 3 V, what does V<sub>2</sub> read?

**V<sub>2</sub> reads 3V since the bulbs are identical each bulb gets the same share of the voltage.**


- (b) Hence, calculate the voltage supply.

$$\mathbf{V_s = V_1 + V_2 \quad \text{therefore} \quad V_s = 3 + 3 = 6V}$$

- (c) The reading on ammeter A<sub>2</sub> is 1 A, what will the reading be on A<sub>1</sub>?

**The current is the same at all points in a series circuit therefore A<sub>1</sub> will read 1 A.**

## Parallel Circuit

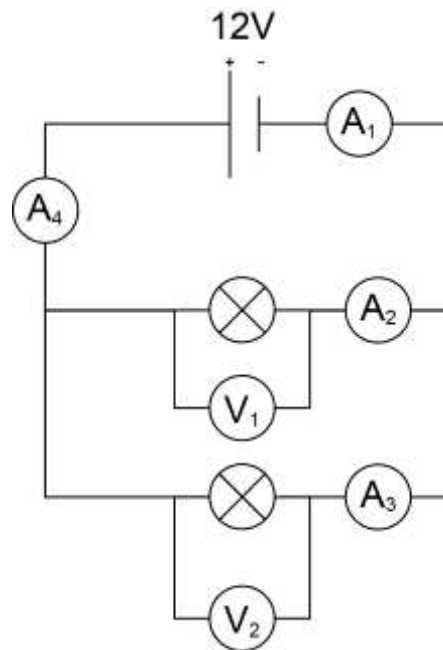

All bulbs are identical

- (a) What are the readings on voltmeters V<sub>1</sub> and V<sub>2</sub>?

**Both read 12 V, since in parallel each branch of the circuit receives the same voltage as the voltage supply.**

- (b) If A<sub>1</sub> reads 3A, calculate the readings on A<sub>2</sub>, A<sub>3</sub> and A<sub>4</sub>.


**The current will split equally between both branches since the bulbs are identical.**

**Therefore, A<sub>2</sub> and A<sub>3</sub> will both read 1.5A.**

**A<sub>4</sub> will read 3A since this is the point in the circuit where the current recombines.**

N5

## Combined series and parallel circuits

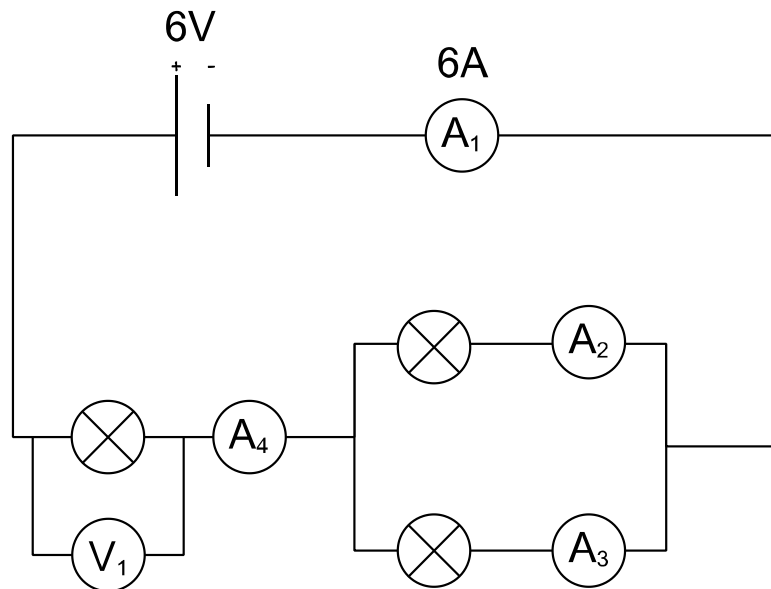

All bulbs are identical

- (a) A<sub>1</sub> reads 6A, what are the readings on A<sub>2</sub>, A<sub>3</sub> and A<sub>4</sub>?

**A<sub>2</sub> and A<sub>3</sub> = 3A, since the supply current is split between both branches equally.**

**A<sub>4</sub> = 6A, at this point the current recombines.**

- (b) What is the reading on V<sub>1</sub>?

**The parallel arrangement of bulbs will have half the resistance of the single bulb.**

**Therefore the parallel bulbs will receive only half the voltage the single bulb will get.**


**V<sub>1</sub> will read 4V and each bulb will receive only 2V.**

[This is explained under the heading resistance in parallel]

N5

## Calculations involving resistors in series and parallel.

### Resistors in Series

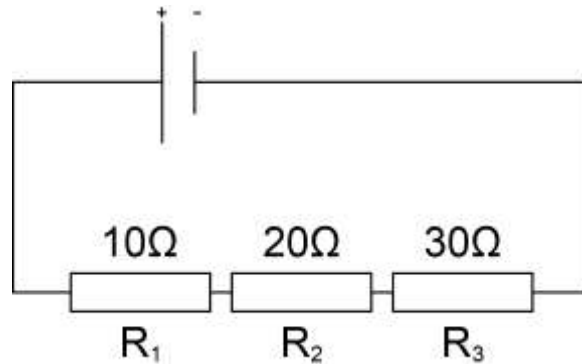


The **total resistance** of all three resistors in series is calculated using the following equation:

$$R_T = R_1 + R_2 + R_3$$

$$R_T = 10 + 20 + 30$$

$$R_T = 60 \Omega$$

### Resistors in Parallel

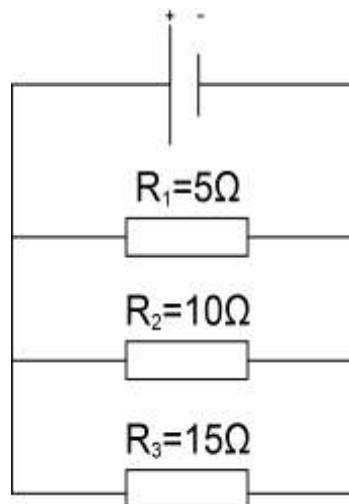

The **total resistance** of all three resistors in parallel is calculated using the following equation:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Therefore

$$\frac{1}{R_T} = \frac{1}{5} + \frac{1}{10} + \frac{1}{15}$$

- Multiply both the top and bottom of each fraction to make all the denominators the same.

$$\frac{1}{R_T} = \frac{6}{30} + \frac{3}{30} + \frac{2}{30}$$

- Add fractions


$$\frac{1}{R_T} = \frac{11}{30}$$

- Invert to calculate  $R_T$

$$\frac{R_T}{1} = \frac{30}{11} = \mathbf{2.72\Omega}$$
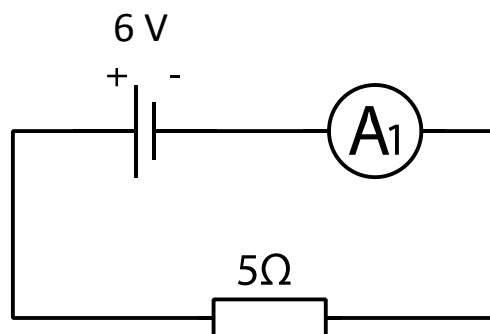
### More on resistors in parallel

Shown below is a simple series circuit complete with a  $5\Omega$  resistor.



Calculate the value of current through the resistor.

$$\left. \begin{array}{l} V = 6\text{ V} \\ R = 5\ \Omega \\ I = ? \end{array} \right\}$$


$$V = I \times R$$

$$6 = I \times 5$$

$$6/5 = I$$

$$I = \mathbf{1.2\text{ A}}$$

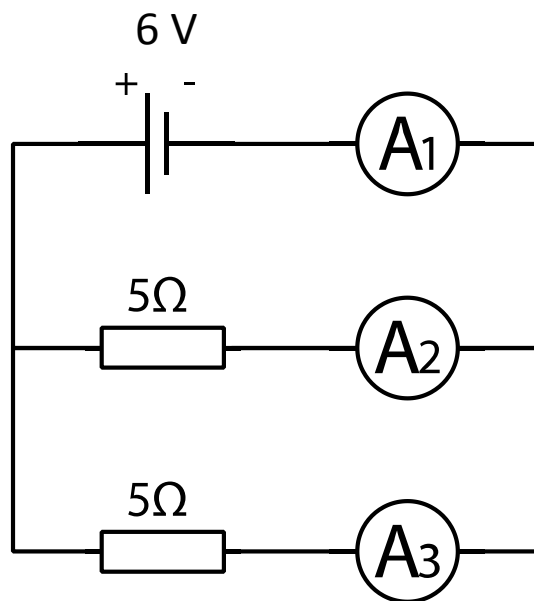Now add another 5 Ω resistor in parallel to the original, the circuit now looks like:



Calculate the value of the current through ammeter A<sub>1</sub>.

- To do this the total resistance of the circuit must be calculated first.

**Step 1**

- $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$

$$\frac{1}{R_T} = \frac{1}{5} + \frac{1}{5}$$

$$\frac{1}{R_T} = \frac{2}{5}$$

$$R_T = 2.5 \Omega$$


**Step 2**

$$V = I \times R$$

$$6 = I \times 2.5$$

$$6 / 2.5 = I$$

$$I = 2.4 \text{ A}$$

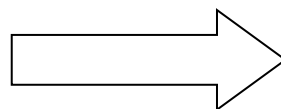

This result shows that when another resistor is added in parallel the total resistance of a circuit is decreased and the current in the circuit is increased.

i.e. by adding an identical resistor in parallel the resistance has halved and the current drawn doubled.