
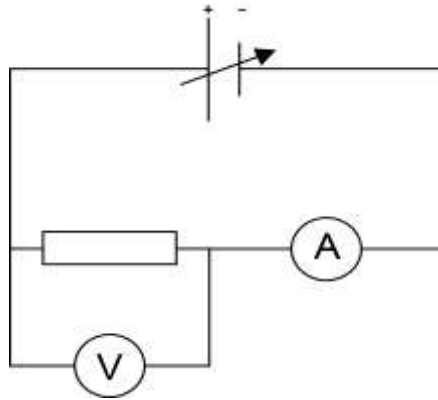


Determining the relationship between V (p.d), current and resistance

N5

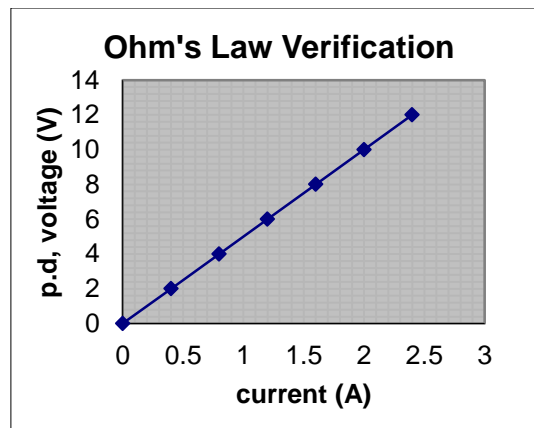

- Using a fixed value of resistor, vary the voltage supply to the circuit.
- Measure and note the values of voltage and current.
- Draw a graph of p.d against I, as shown below



This graph shows that

$$V \propto I$$

$$V = I \times \text{constant}$$

$$\frac{V}{I} = \text{constant}$$

This constant =
gradient of the line

Pick values of potential difference and current from the graph to show that: $V/I = \text{constant}$.

Potential difference (V)	Current(A)	V/ I = constant
2	0.4	5
4	0.8	5
6	1.2	5
8	1.6	5
10	2.0	5
12	2.4	5

Which quantity from the experiment is equal to a constant value of 5?

➤ **The size of the resistor.**

Therefore $\frac{V}{I} = R$ and rearranged gives

$$V = I \times R$$

volts, V ohms, Ω amperes, A

Carry out calculations using $V = I \times R$

Example 1

A mobile phone has a resistance of 4Ω and a current of 3 A passing through it, calculate the size of voltage it uses.

V = ?	}	$V = I \times R$
R = 4Ω		$V = 3 \times 4$
I = 3A		$V = 12 \text{ V}$

Example 2

The lamp has a voltage of 230 V and a resistance of 83Ω , calculate the current passing through the lamp.

V = 230V	}	$V = I \times R$
R = 83Ω		$230 = I \times 83$
I = ?		$\frac{230}{83} = I$
		$I = 2.8 \text{ A}$

Example 3

An electric fire has a voltage of 230 V and a current of 5 A, calculate the resistance of the fire.

$$\begin{array}{l} V = 230\text{V} \\ R = ? \\ I = 5\text{A} \end{array} \left. \vphantom{\begin{array}{l} V = 230\text{V} \\ R = ? \\ I = 5\text{A} \end{array}} \right\}$$

$$V = I \times R$$

$$230 = 5 \times R$$

$$\frac{230}{5} = R$$

$$46$$

$$R = 46 \Omega$$