
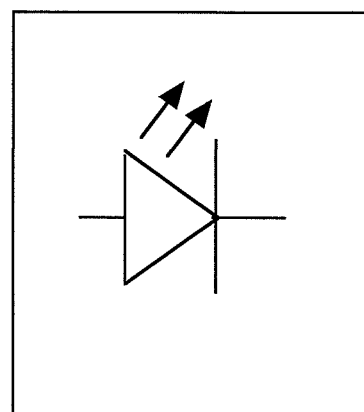
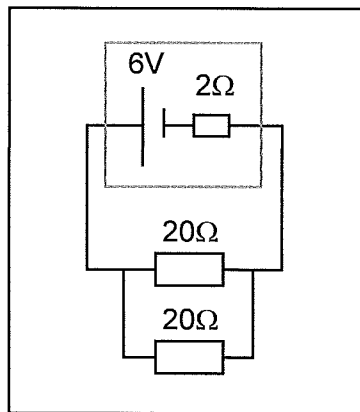


Higher Physics

Unit 3

Electricity


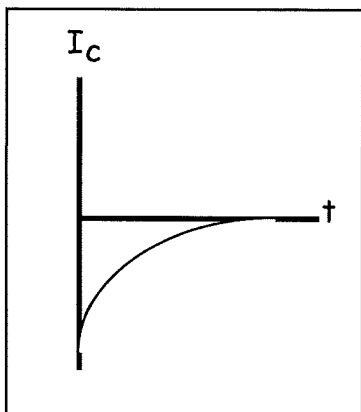


Summary Notes

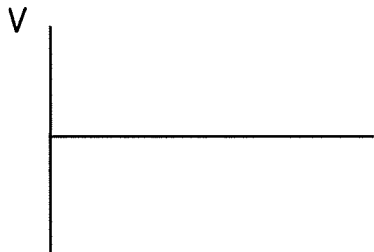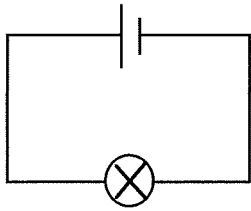1. A.C/D.C



Direct Current d.c

In d.c circuits the voltage is a constant size and _____ so the current is a constant size and _____



Alternating Current a.c

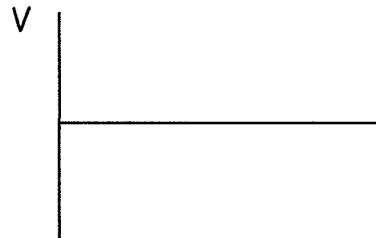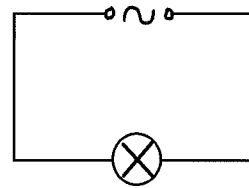
In a.c circuits the size and direction of the voltage is a constantly _____ so the size and direction of a.c current is constantly _____



Measuring ac current and voltage.

Measuring dc current and voltage is easy because they are constant. But to measure ac current or voltage we can describe them by their max value or average or root mean square values (rms) The rms is about 70% of the peak.

V_{ac} or I_{ac}

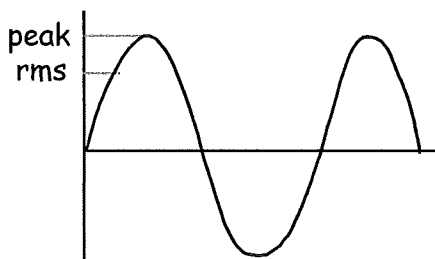

$$V_{rms} = \frac{V_{peak}}{\sqrt{2}}$$


$$I_{rms} = \frac{I_{peak}}{\sqrt{2}}$$

When we use equations such as $V=IR$, $P=IV$ $P = I^2R$ the values of I and V are always the _____ values so remember to convert peak to rms


Measuring peak rms voltage of an ac signal

The Y- gain button on the oscilloscope tells you the value of each _____ box on the screen. If it is set at 5V/cm each vertical box = _____.

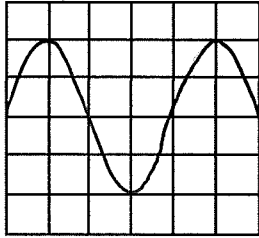So peak voltage = height of the trace x Y- Gain setting.



Y-Gain

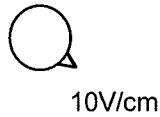

Peak voltage = _____ x _____

Peak voltage = _____ V

Therefore $V_{rms} = \frac{V_{peak}}{\sqrt{2}} = \frac{\quad}{\quad} =$

Measuring the frequency of an ac signal


The frequency tells you how many times the current changes direction each _____. Mains ac electricity has a freq of _____ Hz. So current in household bulbs changes direction _____ times each _____.

The time base tells you how long it takes the electron beam to travel across one horizontal box. So the time to make one wave as it travels across the screen is called the period of the wave or T for short .


Period of wave = time base setting x number of horizontal boxes making one wave.

Frequency $f = \frac{1}{T}$

Period = TB setting x no of horiz boxes

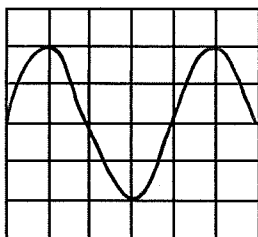

Time base

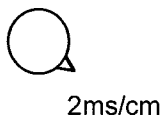

T = _____ x _____


T = _____ s

Freq = $\frac{1}{T} = \frac{1}{\quad} =$

If you increase the y gain setting, the amplitude of the wave on the screen will _____. If you increase the time base setting the beam travels across the screen _____ so _____ waves will be drawn in this time.

2. Circuits


Series

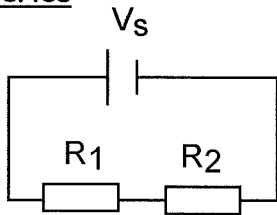

Current at all points is _____.
Voltage across components adds up to the _____ voltage V_s .

$$R_T = R_1 + R_2 + R_{\dots}$$

Ex

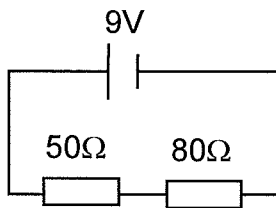

What is the total resistance?
 $= R_T = \underline{\quad} + \underline{\quad} = \underline{\quad} \Omega$


What is the total current?

$$V=IR \text{ so } I = \underline{\quad} = \underline{\quad} =$$


What is the voltage across 50Ω resistor?

$$V_{50} = IR = \underline{\quad} \times \underline{\quad} =$$

$$V_{80} = \underline{\quad}$$

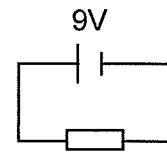

Parallel

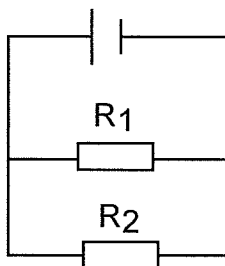


Current in each branch adds up to the _____ current drawn from the battery.
Voltage across each branch is the _____ and equal to the _____ voltage

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

If the resistors are of the same value the total resistance = the size of the resistor / the number in parallel.

Ex

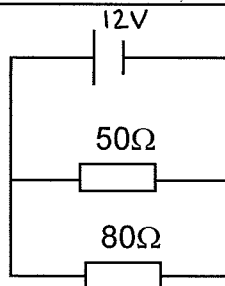


What is total resistance R_T $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{\quad} + \frac{1}{\quad} =$

$$\text{So } R_T = \quad =$$

What is total current

$$V=IR \text{ so } I = \quad = \quad =$$


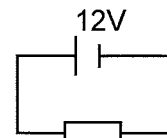
What is current through 50Ω resistor $V = IR$ so $I = V/R =$



Resistors in parallel with same value


$$R_T = \frac{\text{value of resistor}}{\text{number in parallel}}$$

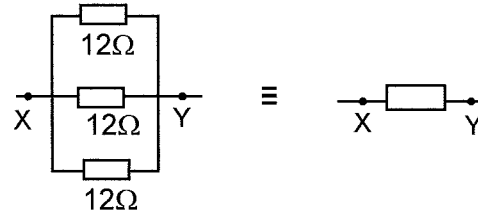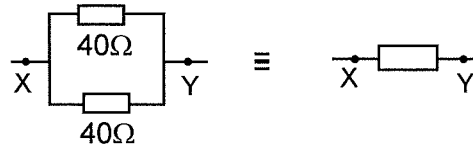What is total resistance between X and Y in these circuits



Combined Series and parallel circuits.

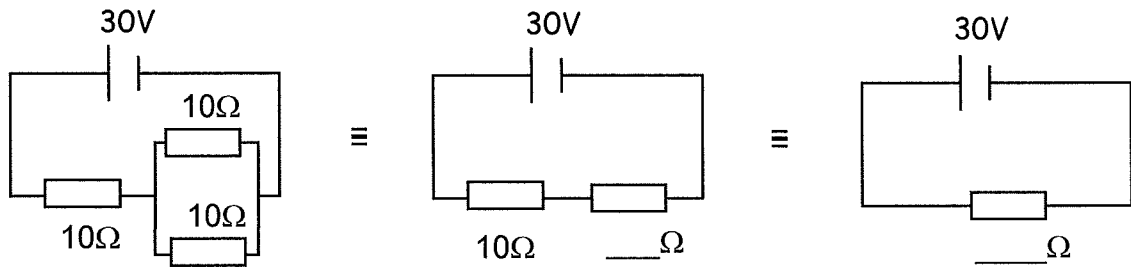Work out (a) total resistance (b) Total current (c) Voltage across 10Ω resistor




$$V_{10} =$$

$$I_T = \frac{V_T}{R_T} = \frac{\quad}{\quad} =$$

The voltage divider formula

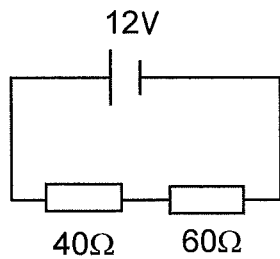This formula allows you work out the voltage across resistors in series much more quickly than finding the total resistance then current.




$$V_1 = \frac{R_1}{R_1 + R_2} \times V_s$$

$$V_{40} = \quad \times 12$$

$$V_{40} = \quad \times 12$$


$$V_{40} = \quad \quad \quad \text{so } V_{60} =$$

Also for a voltage divider-

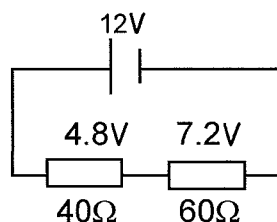


$$\frac{R_1}{R_2} = \frac{V_1}{V_2} \quad \quad =$$

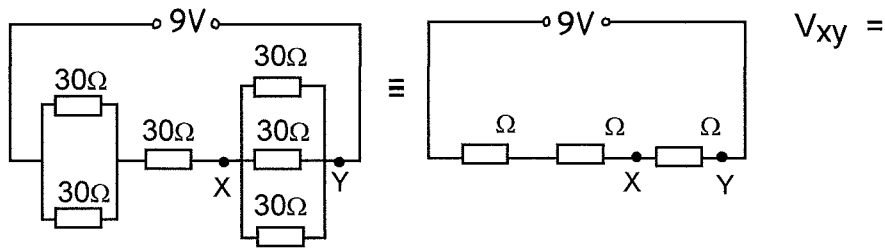Ex What is the voltage between X and Y? - Simplify and use the voltage divider formula.



When resistors are placed in parallel the total resistance of the circuit

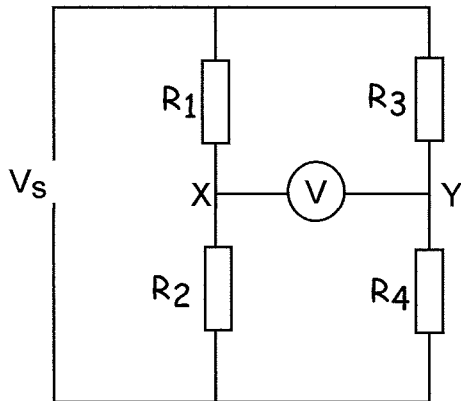
Two facing potential dividers (Wheatstone Bridge)



Resistors can be chosen so the pd at X = pd at Y. This is called a balanced circuit. In a balanced circuit -

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

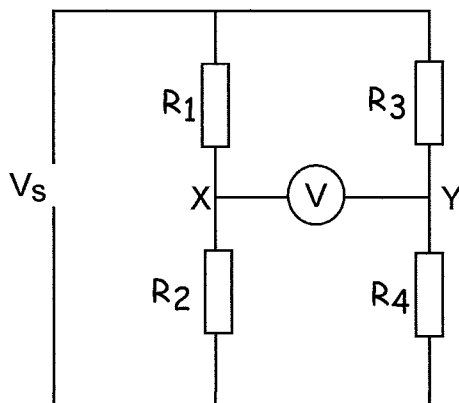In an out of balanced circuit we can find voltage at X and Y and calculate the pd between X and Y. (Measured on voltmeter)



$$V_X = \frac{R_2}{R_1 + R_2} \times V_s$$

$$V_Y = \frac{R_4}{R_3 + R_4} \times V_s$$


$$V \text{ read by voltmeter} = V_X - V_Y$$

Ex What is voltage at X?

$$V_X = \text{---} \times 8 = \text{---} \times 8 =$$

What is voltage at Y? $V_Y = \text{---}$

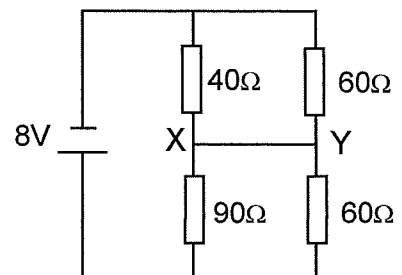Potential difference between X and Y = ---



Power

The electrical power of a device tells you the amount of electrical _____ the device uses each second. Here are 3 useful equations:

$P = IV$

$P = I^2R$

$P = \frac{V^2}{R}$


Internal Resistance

An electrical battery or cell uses a chemical reaction to drive current round the circuit. But some energy is always lost in the process.

Emf (E) = Electromotive _____ of the cell. This is the maximum amount of _____ energy given to each coulomb. It is the max available voltage.

lost volts (v)= The voltage _____ inside the cell due to driving the current. This lost voltage is turned to _____ in cell. We imagine it dropped across an internal _____ (r).

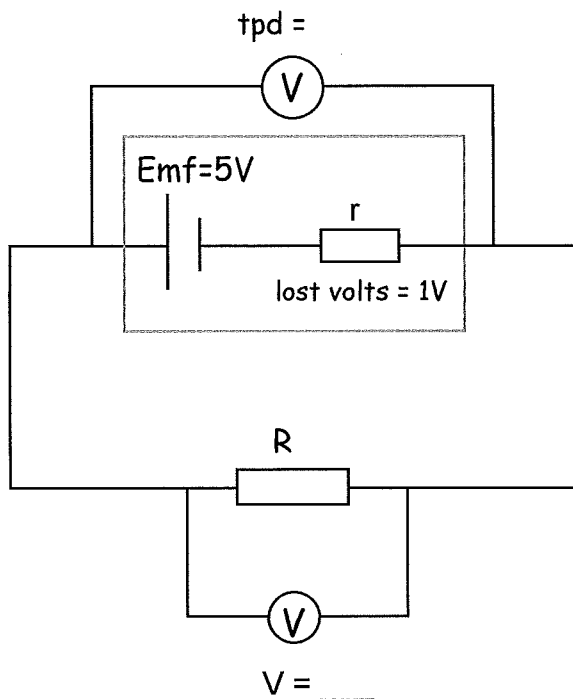tpd (V) = terminal _____ difference. This is the actual voltage measured across the cell once you have taken lost volts away from the _____. This tpd is dropped across the external load which we denote as R.



$tpd = Emf - \text{_____}$


$tpd = \text{_____} - \text{_____}$

The tpd is _____V. This is the voltage available to the external load. So the voltage across R =

Big R and small r are in series so the total resistance of circuit = ____ + ____.

We can also use the voltage divider formula to find lost volts or tpd.

Graphical method of measuring E and r

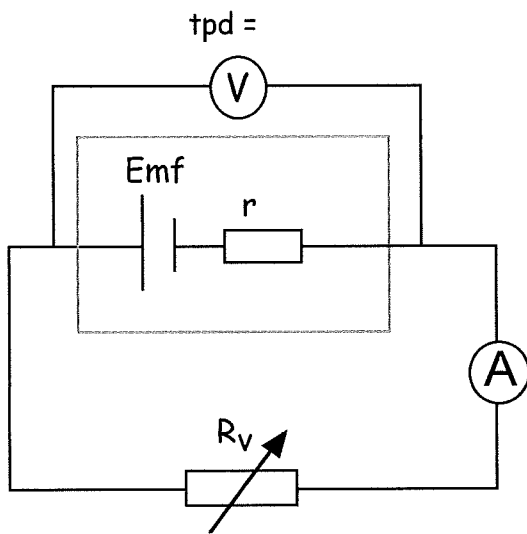

$$E = \text{tpd} + \text{lost volts}$$

$$E = V + Ir$$

$$V = -Ir + E$$


$$V = -rI + E$$

$$y = mx + c$$

So plotting I vs V gives a straight line where $r = -\text{gradient}$ and it cuts y axis at $(0, E)$

Set variable resistor to a high value. Therefore current drawn is _____
So as lost volts $v=Ir$ the lost volts will also be small. Therefore the tpd will be _____

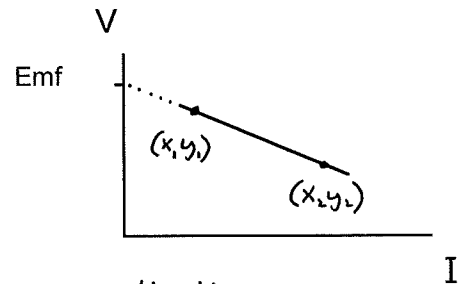As R is decreased the current _____ so
the lost volts _____ and the
tpd _____. If we plot
I vs V the graph looks like this




gradient = $-r$ & y-intercept = _____

Ideal supply

$$\text{gradient } m = \frac{y_2 - y_1}{x_2 - x_1}$$



The maximum power transferred to a load is when the load resistance R = the _____ resistance r. This is called Load _____.

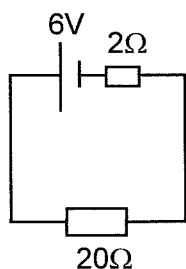In many applications placing more and more external resistors in parallel _____ the total resistance of the circuit. Therefore the current drawn from the battery _____ so as lost voltage $v=Ir$ the lost voltage _____ and the useful voltage or tpd _____.



$$\text{tpd} = V_{20\Omega}$$

$$V_{20\Omega} = \text{---} \times 6$$

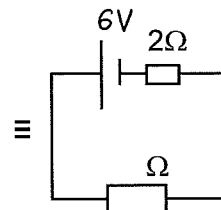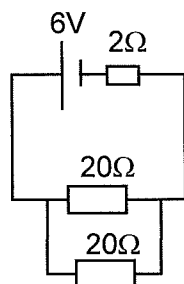


$$\text{tpd} = V \ \Omega$$

$$V \ \Omega = \text{---} \times 6$$

Short Circuit

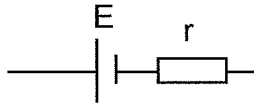A short circuit is created when a wire provides a short cut for electricity to flow directly from one side of the _____ to the other by missing out the load resistor.






so short circuit current $I_{SC} = \frac{E}{r}$

Open circuit

An open circuit is one where no current flows in the circuit. As there is no current then there is no lost voltage (ie $v=Ir$, $I=0$ so $v=0$). So tpd = _____.

Capacitors

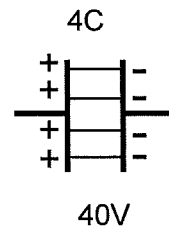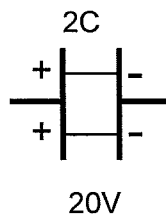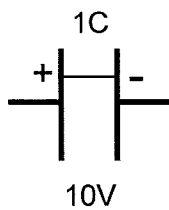A capacitor is a device which stores _____ on two metal plates. This creates an electric field between the plates which stores electrical _____. As we place more charge on the plates the pd or voltage between the plates _____, as shown on the diagrams and graph.



The area under the QV graph tells us the amount of electrical _____ stored on the capacitor

$E =$

Dividing Q by V gives us a constant which we call the _____ of the capacitors.

$$C = \frac{Q}{V}$$

Q = charge, units - Coulombs C

V = voltage, units volts V

C = capacitance, units - Farads F

A Capacitance of 5F means you need to put ___C of charge on plates to create a pd of 1V.

Substituting this equation into the energy equation gives us two more equations for the energy stored on a capacitor.


$$E =$$

$$E =$$

Different sizes of capacitors


As a capacitor gets bigger it takes more _____ to produce a pd of 1V.

Small capacitor

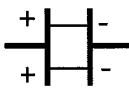


takes 2C to produce 1V
so $C = 2F$

Medium capacitor

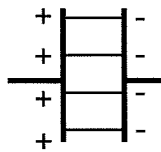


takes 4C to produce 1V
so $C = 4F$

Big capacitor

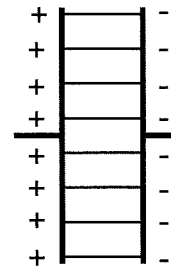


takes 8C to produce 1V
so $C = 8F$

Charging a Capacitor

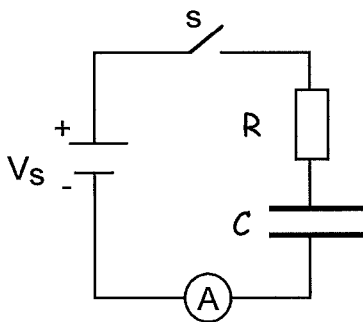


When switch S is closed, the top plate of the capacitor becomes very _____ charged so there is a huge attraction for electrons to flow onto the bottom plate. At first the current rises very _____ because the attraction is very _____. But as time passes the electrons already on plate start repelling electrons arriving at plate so the current _____ until no more electrons can get on. At this point the capacitor is fully charged and its voltage = _____. Current is now _____.

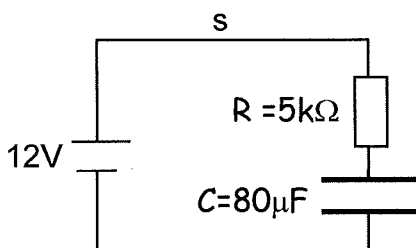At all points during charging $V_S = V_R +$ _____



When fully charged $V_C =$ ____V


Energy stored =

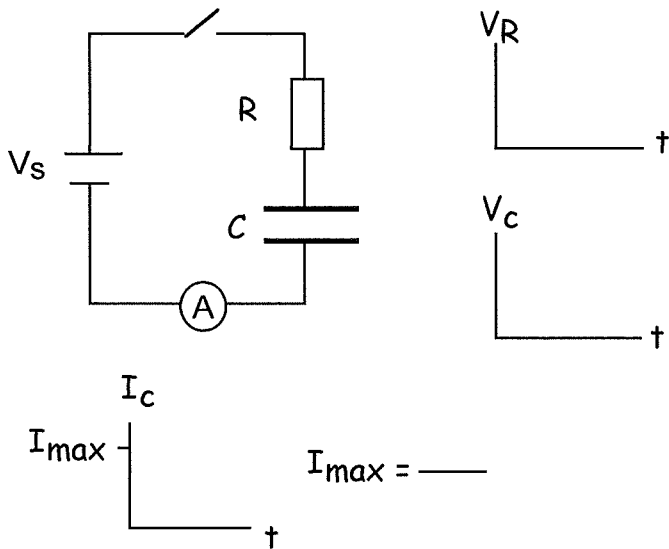


Just as switch is closed all voltage is dropped across _____ because capacitor is empty. At this point current is maximum. $I_{max} = V_s/R$. This is called the initial charging current. As time goes by the voltage across the capacitor _____ as it charges up. The voltage across the resistor decreases. When the capacitor is fully charged the voltage across the capacitor = the _____ voltage. At this point the current = _____ and $V_R =$ _____

Discharging a Capacitor

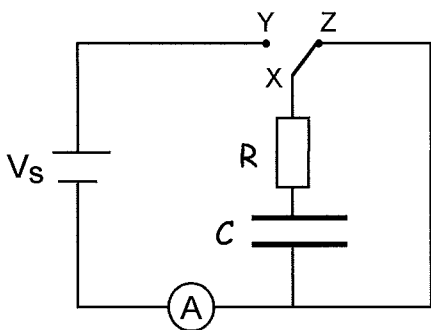
When X is connected to Y the capacitor _____ up through R. When fully charged it is full of electrical _____, and $V_c =$ _____. When X is connected to Z the capacitor discharges through R and electrons now have a path to get round to positive plate.



discharging graphs

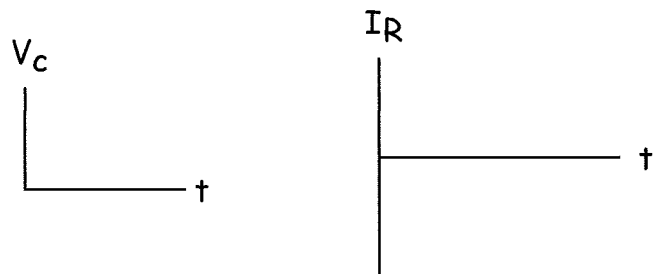

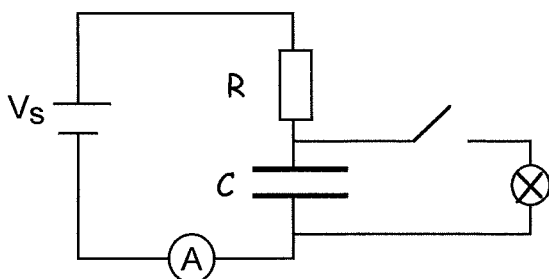If the capacitor is discharged very quickly all this energy can be converted to another form very quickly. For instance a camera's _____ or the pads on a hospital _____ machine. As power is energy per second a small amount of energy delivered in a short time can create a _____ power output.



Energy stored on fully charged capacitor-

$$E = \frac{1}{2}CV^2$$

$$\text{Power output } P = \frac{E}{t}$$

Changing R and C


Increasing R means that it is more difficult for _____ to flow round the circuit therefore it takes _____ for the capacitor to charge up and _____ for it to discharge.

Changing R has _____ effect on the final voltage and charge stored on capacitor.


Increasing C means that it takes _____ for the capacitor to charge up and _____ for it to discharge.

If Capacitance increases then it will take _____ charge to reach the max voltage. $C = Q/V$ so that is why it takes longer.


Charging

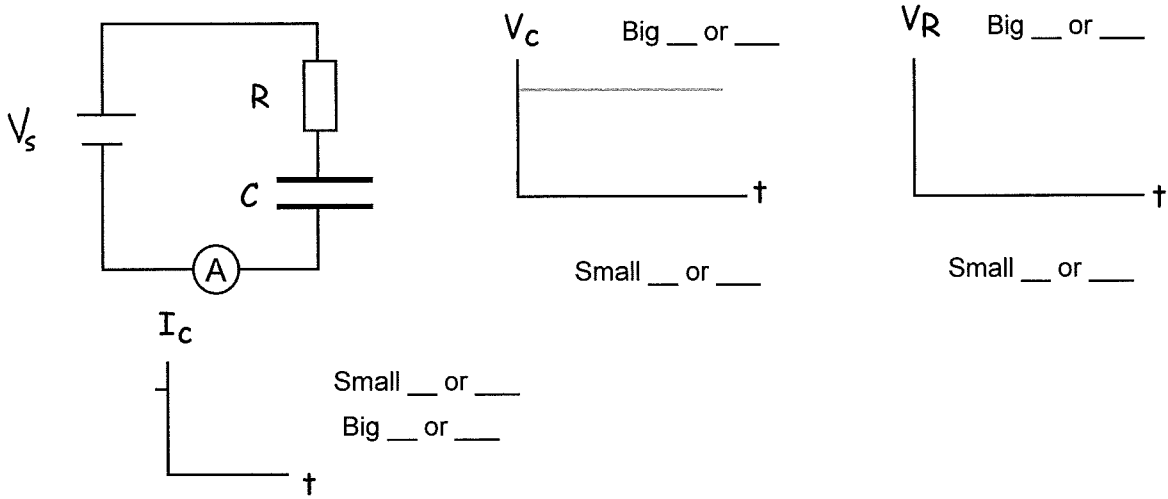

Discharging

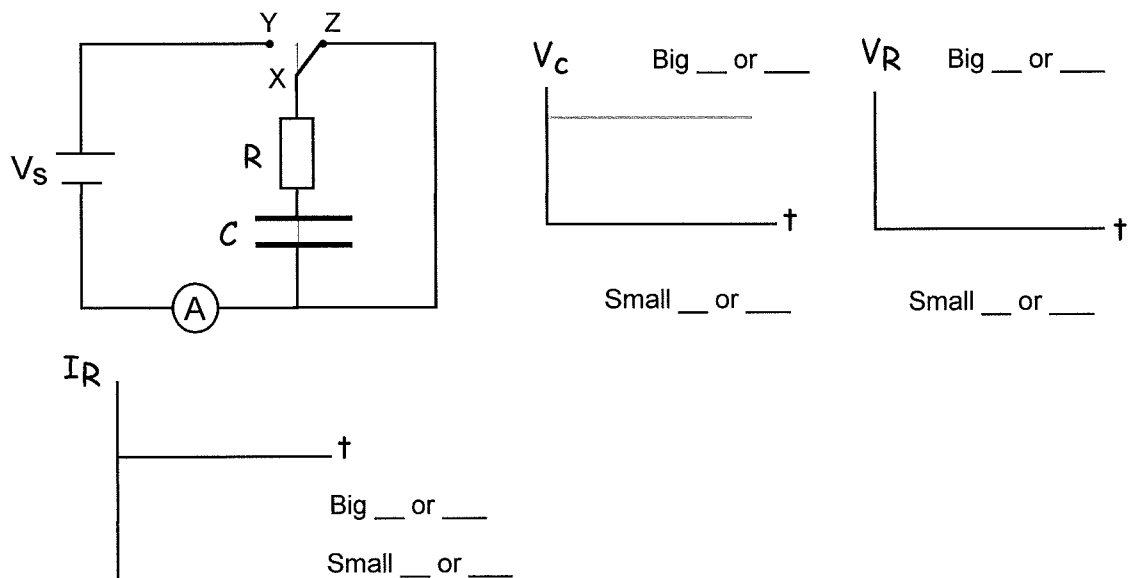

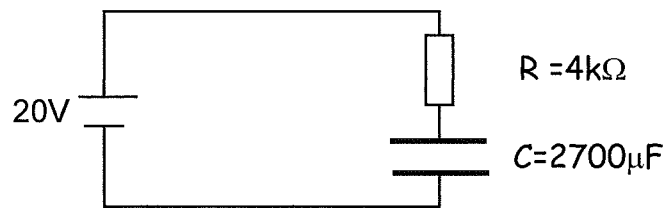Ex The following circuit was set up to charge a capacitor.




(a) Calculate the initial charging current.

(b) At one point the current in the circuit is 2mA. What is the voltage across the capacitor at this point?

(c) Calculate the charge stored on the plates of the capacitor when it is fully charged.


(d) Calculate the energy stored on the capacitor when it is fully charged.

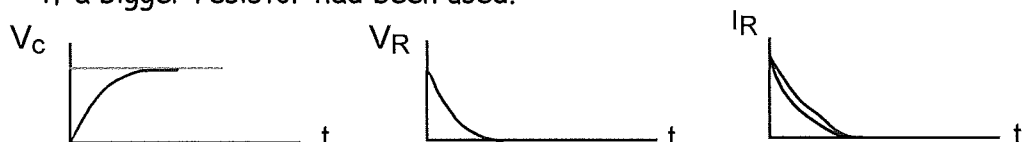(e) Below are the graphs showing voltage across capacitor and resistor and current through resistor during charging. Draw trace which you would get if a bigger resistor had been used.



Semiconductors

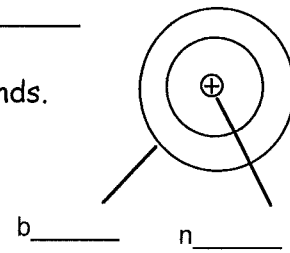
An atom is made up from a nucleus containing positive p _____ and n _____ which have no c _____.
Electrons can only exist in discrete e _____ levels or bands.
Electrons fill the bands nearest to the n _____.



Electrons which break free of the atom are said to be in the c _____ band.


Insulators

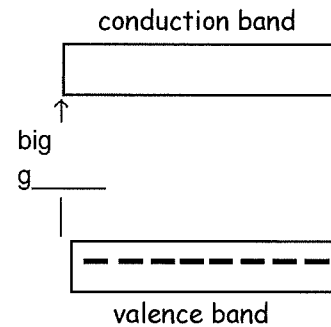In insulators the highest occupied band is the v _____ band. There are no free e _____ so there are no electrons in the c _____ band. Even h _____ will not cause electrons to move from the v _____ to the c _____ band as there is a big band g _____.




Conductors

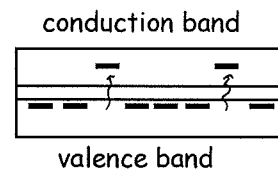In conductors like metals the valence band is n _____ full so this allows electrons to move into the c _____ band. From here they can move from atom to atom if a pd is applied. Bands o _____.



Semiconductors

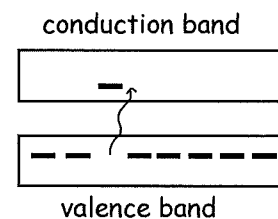Semiconductors are materials where the valence band is c _____ to the conduction band so the addition of heat or voltage can cause electrons to move from the v _____ band to the conduction band thus increasing its c _____.



The conductivity of a semiconductor can be further i _____ by d _____.


Doping

A pure or intrinsic semiconductor can be made from s _____ or germanium and are insulators at r _____ temperature. They each have _____ electrons in their valence band. So to create a full valence band it requires to bond with another atom with _____ outer valence electrons.

Doping is the process of adding an i _____ atom to a pure semiconductor. This has the effect of increasing the semiconductor's c _____ and decreasing its r _____.

n-type semiconductor.

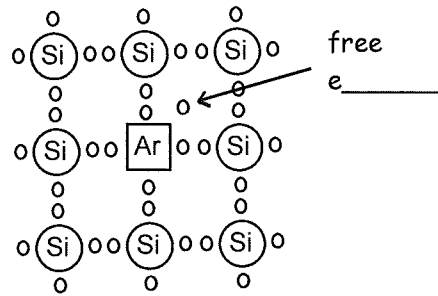
Atoms in a silicon atom have 4 outer electrons. An Arsenic atom has 5 outer electrons. So if the Si is doped with an Ar atom 4 electrons in each atom bond which leaves a free electron which moves into the conduction band.



We say that the majority charge carrier in an n type semiconductor are negative electrons.


p-type semiconductor.

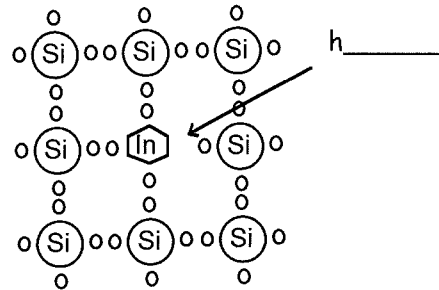Atoms in a silicon atom have 4 outer electrons. An Indium atom has 3 outer electrons. So if the Si is doped with an In atom 3 electrons in the Si outer band bond with the 3 electrons in the Indium atoms outer band. This leaves a space or hole where an electron should be. We treat this hole as a Positive charge carrier



We say that the majority charge carrier in an p type semiconductor are positive holes.


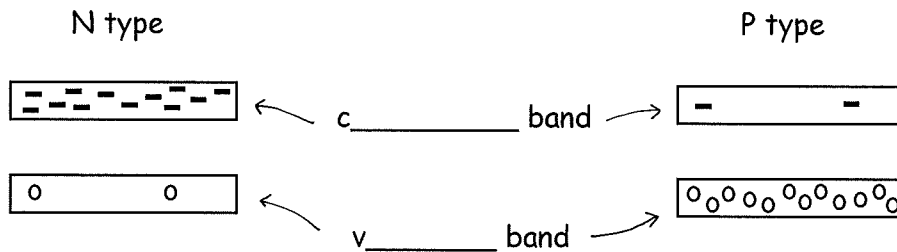
Energy band diagram for a n and p type semiconductor



N and p type semiconductors are still electrically neutral as every electron present is balanced by a proton in the atom's nucleus

PN junction diode

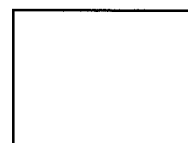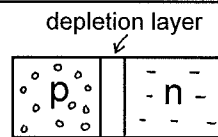When a p type and an n type semiconductor are grown together we create a pn junction diode. An area at the junction is formed called the depletion layer. There are no carriers in this layer.




Draw the symbol for a pn junction diode here

Biasing

When a voltage is applied to a diode it can either be forward or r_____ biased

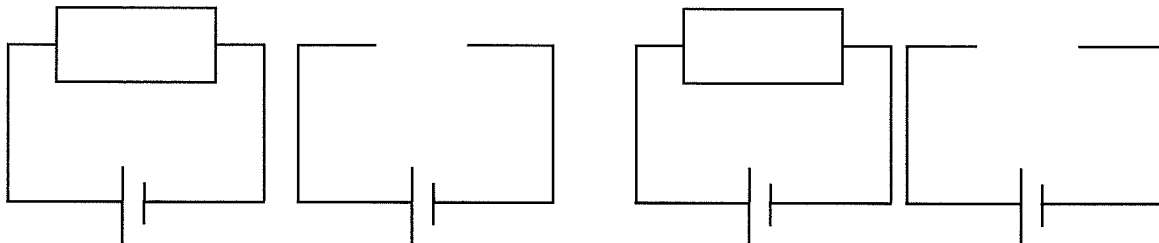
F_____ bias - charges are pulled a_____ junction and a current flows
 R_____ bias - charges are pulled a_____ from junction and no current flows



The photodiode

When a piece of clear plastic is placed over the depletion layer p_____ of light can enter the diode. The photons hit the depletion layer and produce e_____ h_____ pairs. This has the effect of increasing the emf across the d_____ layer. This emf can be used as a source of electrical e_____. The brighter the light the bigger the e_____.

Draw the symbol for a photodiode here

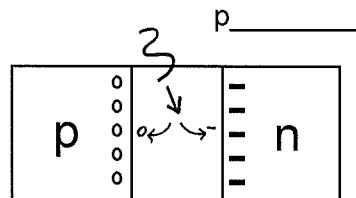

This is called the p_____ effect because photons are being used to produce a v_____ or emf. The photodiode is acting as a solar c_____.

Calculating pd across junction

A photon of frequency $6.8 \times 10^{14} \text{ Hz}$ is incident on a photodiode.
 What is the maximum voltage this photon can produce across the junction?

Light emitting diode LED

When a photodiode is placed in a f_____ biased circuit electrons and holes are pulled across the junction. Occasionally they meet and r_____. This recombination produces a p_____ of light. The distance between the conduction and valence band determines the c_____ of light produced.



Draw the symbol for a photodiode here



These two diagrams show a photodiode in forward bias.

Draw the symbol for a photodiode in forward bias

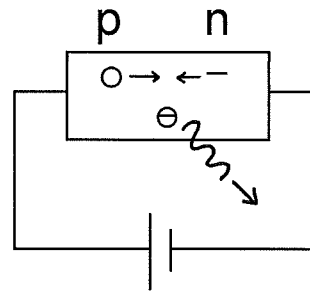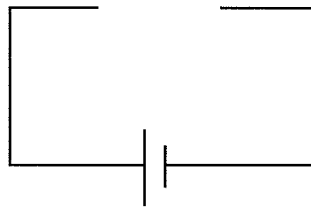
hole and electron r_____ and produce a p_____



The recombination energy when an electron and hole meet is $4 \times 10^{-19} \text{ J}$

- (a) Calculate the frequency of the emitted photon.
- (b) Calculate the wavelength of the emitted photon.

Energy band diagram for an LED

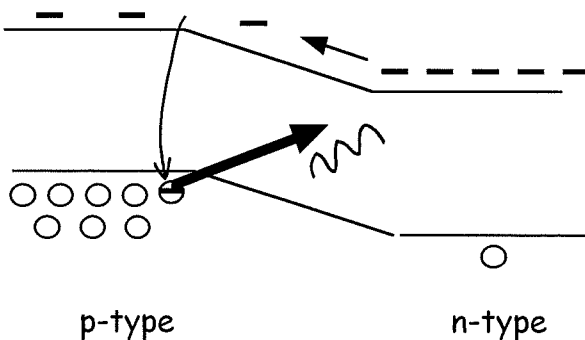

electron moves across junction in the c_____ band. Once across they fall into valence band and recombines with a h_____.